

# **GATE CSE NOTES**

by

**UseMyNotes**

\* Signal: A function that represents the variation of a physical quantity with respect to any parameter.

In Electronics, usually signal is variation of electrical quantity (current or voltage) with time.


If  $dI = 0$ , then  $I$  is not a signal; it's DC.

\* Transducer: Used to convert non-electrical signal to electrical signal.


Reverse Transducer: Used to convert electrical signal to non-electrical signal.

\* Analog Signal: A continuous function that is existent for any value of independent variable.

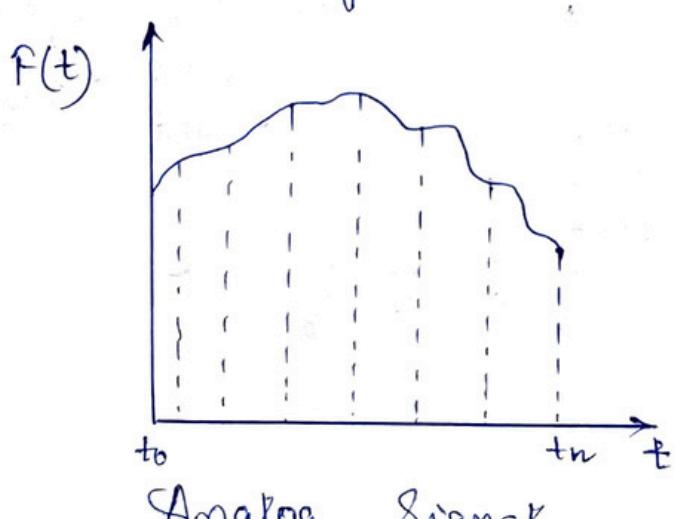\* Discrete Time Signal: Signal defined for discrete intervals of time.



Analog Signal

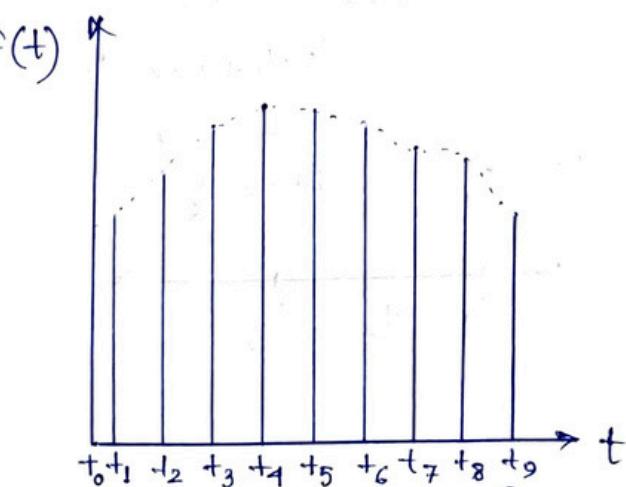


Discrete time Signal.

## \* Signal types :

- Discrete time, continuous amplitude
- Discrete time, discrete amplitude
- Continuous time, continuous amplitude
- Continuous time, discrete amplitude.

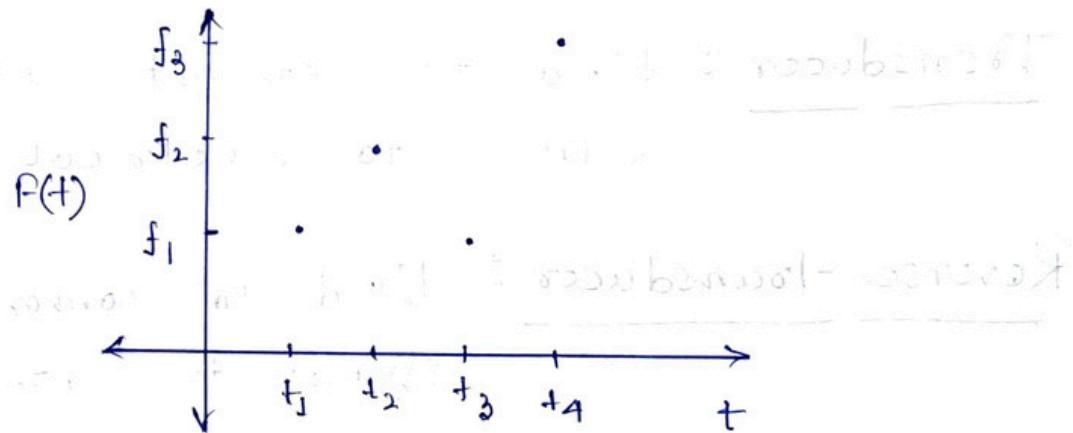
## \* Digital Signal : Discrete time, discrete amplitude signal.


Signal can take certain values due to discretisation of amplitude.



More the number of levels, lesser the error.
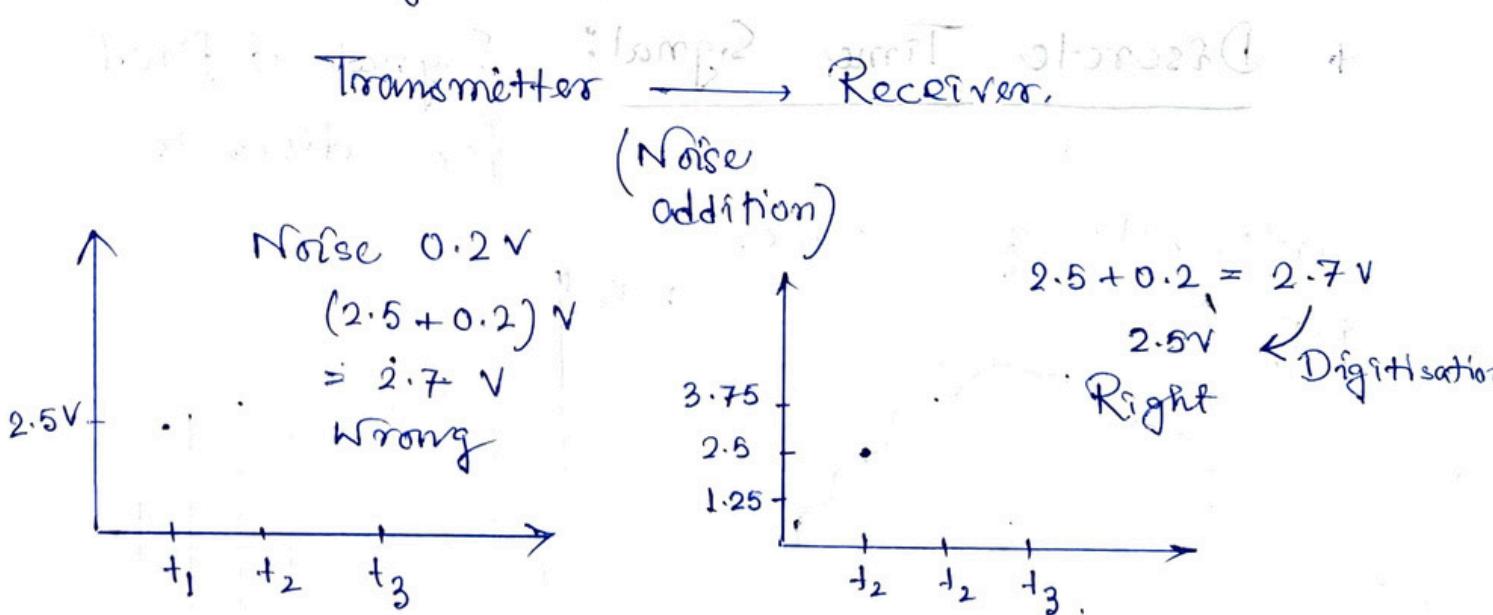
## \* Need of Digital Signal : Digital signal is used to minimise the effect of noise.



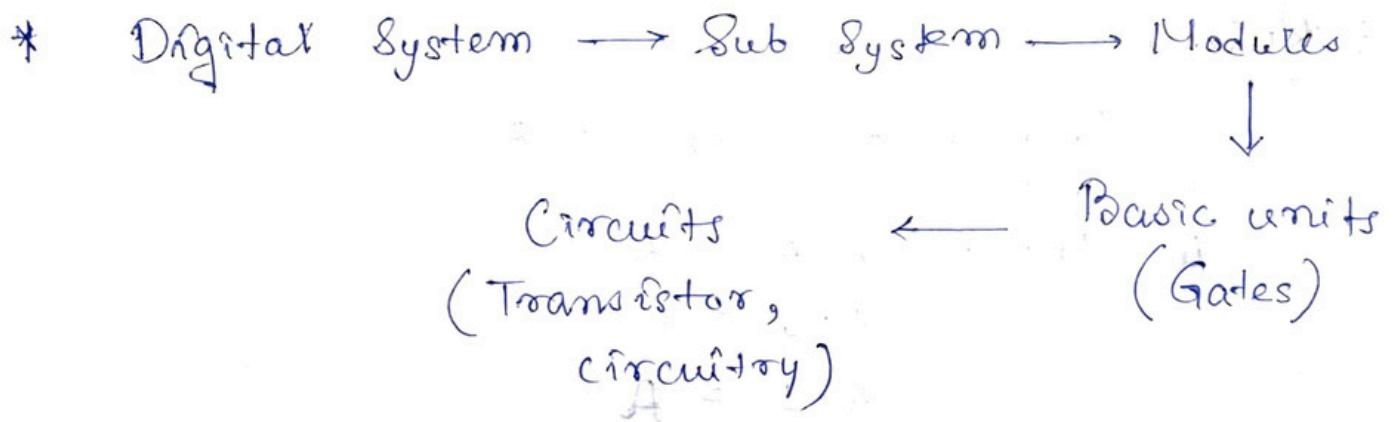

## \* Advantages of Digital Systems:

- i) Noise immunity
- ii) Uses less bandwidth
- iii) Encryption.
- iv) Efficiency for long distance transmission

## \* Switch & Bits :

- |            |          |     |    |
|------------|----------|-----|----|
|            |          | OFF | ON |
| 1 switch   | 2 Level  | 0   | 1  |
| 2 switches | 4 Levels |     |    |
- m switches  $2^m$  levels.  $[x = 2^m]$ .
  - bits - 0 & 1. used to represent switch.

\* Boolean Algebra: Set of rules, used to simplify the given logic expression without changing functionality.

Used when number of variables are less.

For more variables, we use K-Map.

The final simplified result in Boolean Algebra is not always same (drawback).

## \* Rules :

i) Complement :  $(A')' = A$

ii) AND :  $A \cdot A = A$

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A \cdot A' = 0$$

iii) OR :  $A + A = A$

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + A' = 1$$

iv) Distributive :

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$* A + (B \cdot C) = (A + B) \cdot (A + C)$$

$$\left\{ \begin{array}{l} A + A'B = A + B \\ A + AB = A + B \end{array} \right.$$

v) Commutative :

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

vi) Associative :

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

vii) Priority :

NOT

AND

OR

More

viii) De Morgan's Law :

$$(\overline{A+B}) = A' \cdot B'$$

$$(\overline{A \cdot B}) = A' + B'$$

$$\begin{aligned}
 \text{Eg. 1. } Y &= BAC' + B'AC' + BC' \\
 &= AC'(B + B') + BC' \\
 &= AC' \cdot 1 + BC' \\
 &= AC' + BC' \\
 &= (A + B)C'
 \end{aligned}$$

$$2. AB + AB'$$

$$\begin{aligned}
 &= A(B + B') \\
 &= A \cdot 1 \\
 &= A
 \end{aligned}$$

$$3. AB + AB'C + AB'C'$$

$$\begin{aligned}
 &= A(B + B'C) + AB'C' \\
 &= A(B + C) + AB'C' \\
 &= AB + AC + AB'C' \\
 &= A(B + C + B'C') \\
 &= A(B + B'C' + C) \\
 &= A(B + C' + C) \\
 &= A(B + 1) \\
 &= A \cdot 1 = A
 \end{aligned}$$

$$4. (A + B + C)(A + B' + C)(A + B + C')$$

$$\begin{aligned}
 &= ((A + B) + C \cdot C')(A + B' + C) \\
 &= (A + B + 0)(A + B' + C) \\
 &= (A + B)(A + B' + C) \\
 &= A + B \cdot (B' + C)
 \end{aligned}$$

$$= A + BB' + BC$$

$$= A + BC$$

$$5. (A + B)(A + B')(A' + B)(A' + B')$$

$$\begin{aligned}
 &= (A + B \cdot B')(A' + B \cdot B') \\
 &= A \cdot A' \\
 &= 0
 \end{aligned}$$

## \* Redundancy      Theorem:      Consensus theorem

1. Three Variables

2. Each variable repeated twice.

3. One variable is complemented.

4. Take the complemented Variable.

$$\text{Eg. } Y = AB + A'C + BC \quad \underline{\text{redundant}} \\ = AB + A'C.$$

$$\text{Proof. } (AB + A'C + BC \cdot 1)$$

$$= AB + A'C + BC \cdot (A + A') \\ = AB + A'C + ABC + A'BC \\ = AB(1+C) + A'C(1+B) \\ = AB + A'C.$$

$$\text{Eg. } (A+B) \cdot (\bar{A}+C) \cdot (B+C).$$

$$= (A+B) \cdot (\bar{A}+C).$$

$$\text{Eg. } \bar{A}\bar{B} + A\bar{C} + \bar{B}\bar{C}$$

$$= \bar{A}\bar{B} + A\bar{C}$$

\* Sum of Product: Expression of product when the function is high (1).

<u>minterms</u>	A	B	C	F
$m_0$	0	0	0	0
$m_1$	0	0	1	0
$m_2$	0	1	0	1
$m_3$	0	1	1	0
$m_4$	1	0	0	1
$m_5$	1	0	1	1
$m_6$	1	1	0	1
$m_7$	1	1	1	1

$$F = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + \\ A\bar{B}\bar{C} + ABC, \\ [\text{SOP Form}].$$

Canonical/Standard SOP form  
(derived from Truth table).

- Minterm =  $\bar{A}BC$ ,  $\bar{A}\bar{B}C$  etc.

$$F(A, B, C) = m_2 + m_4 + m_5 + m_6 + m_7 \\ = \sum m (2, 4, 5, 6, 7)$$

Eg.  $F = \bar{A}B\bar{C} + A\bar{B}[C + \bar{C}] + AB[\bar{C} + C]$

$$F = \bar{A}B\bar{C} + A\bar{B} + AB$$

$$F = \bar{A}B\bar{C} + A[B + \bar{B}]$$

$$F = \bar{A}B\bar{C} + A$$

$$F = A + B\bar{C} \quad [\text{Minimal SOP Form}]$$

- Canonical form: Each minterm is having all the variables in normal or complemented form.
- Minimal form: Each minterm does not have all the variables in normal or complemented form.

			minimize SOP expression.
A	B	Y	
0	0	0	
0	1	1	$Y = \bar{A} \cdot B + A \cdot \bar{B}$ .
1	0	0	$Y = B$
1	1	1	

Eg.  $Y(A, B) = \sum m (0, 2, 3)$ .

$$Y = m_0 + m_2 + m_3$$

$$= \bar{A}\bar{B} + A\bar{B} + AB$$

$$= \bar{B} + AB$$

$$= A + \bar{B}$$

## \* Product of Sum (POS Form):

- Used when the output is low (0).

	A	B	C	$Y$	
$M_0$	0	0	0	0	$Y = (A+B+C) \cdot (A+B+\bar{C})$ .
$M_1$	0	0	1	0	$(A+\bar{B}+\bar{C})$ .
$M_2$	0	1	0	1	
$M_3$	0	1	1	0	
$M_4$	1	0	0	1	$0 \rightarrow A$
$M_5$	1	0	1	1	$0 \rightarrow \bar{A}$
$M_6$	1	1	0	1	$1 \rightarrow \bar{A}$
$M_7$	1	1	1	1	$1 \rightarrow A$
				<u>POS</u>	<u>SOP</u>

maxterm =  $A+B+C$ ,  $A+B+\bar{C}$  etc.

$$\bar{Y} = \bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot \bar{C}$$

$$(\bar{Y})' = [\bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} C + \bar{A} B \bar{C}]'$$

By de Morgan's Law,

$$Y = (A+B+C) \cdot (A+B+\bar{C}) \cdot (\bar{A}+\bar{B}+\bar{C})$$

$$Y = [(A+B) + C \cdot \bar{C}] (A + \bar{B} + \bar{C})$$

$$= (A+B) \cdot (A + \bar{B} + \bar{C})$$

$$= A + B \cdot (\bar{B} + \bar{C})$$

$$= A + B\bar{C}$$

$$= (A+B) (A+\bar{C}) \quad \text{Minimal form}$$

Eg. Minimise POS expression.

A	B	$Y$	$Y = (A + \bar{B}) \cdot (\bar{A} + B)$
0	0	1	$= A\bar{B} + \bar{A}\bar{B} + \bar{B}A$
0	1	0	$= A\bar{B} + \bar{B}$
1	0	1	
1	1	0	$= \bar{B}$

$$Y = \prod (M_1, M_3)$$

$= \prod M(1, 3) \therefore$  Maxterm

$$Y = \sum m(0, 2) \quad \text{Minterm}$$

• SOP Form - AND

POS Form - OR

Eg.	A	B	C	Y	$Y(A, B, C) = \sum m(0, 2, 3, 6, 7)$
	0	0	0	1	SOP
	0	0	1	0	$Y(A, B + C) = \prod M(1, 4, 5)$
	0	1	0	1	POS
	0	1	1	1	$Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C +$
	1	0	0	0	$\bar{A}B\bar{C} + A\bar{B}C$ : canonical
	1	0	1	0	$= \bar{A}\bar{C} + B$ minimal
	1	1	0	1	
	1	1	1	1	

POS

$$Y = (A+B+\bar{C})(\bar{A}+B+C)(\bar{A}+B+\bar{C}) \quad \text{canonical.}$$

$$= (B+\bar{A})(B+\bar{C}) \quad \text{minimal}$$

• Minimal to Canonical:

$$Y = A + B'C$$

$$= A \cdot 1 \cdot 1 + B'C \cdot 1$$

$$= A \cdot (B+B') \cdot (C+C')$$

$$+ B'C (A+A')$$

$$= (AB + AB') (C+C')$$

$$+ B'C A + B'C A'$$

$$= ABC + ABC' + AB'C + AB'C' + B'C A + B'C A'$$

SOP

Step 1: 3 Variables

A, B, C.

Step 2:  $m_1 \bar{A} \vee m_2 A \bar{X} \vee m_3 A X \bar{B} \vee m_4 A X B \vee m_5 A \bar{X} B \vee m_6 \bar{A} \bar{X} B \vee m_7 \bar{A} X \bar{B} \vee m_8 \bar{A} \bar{X} \bar{B}$

$\bar{B} X$

$B \vee$

$C X$

$C \vee$

Step 3:  $B + \bar{B} = 1$

replacement

~~B'C A~~

~~B'C A'~~

$$F = (A+B+C') (A'+C)$$

POS

$$= (A+B+C') (A'+C+BB')$$

$$= (A+B+C')$$

$$\{(A'+C)+B\} \{ (A'+C)+B'\}$$

$$= (A+B+C') (A'+B+C) \quad \text{iii)} \\ (A'+B'+C).$$

3 variables

Term 1

A ✓

B ✓

C ✓

Term 2

A ✓

B ✗

C ✓

$$CC' = 0$$

replacement

$$\text{Eg. } f = A + B'C.$$

$$= A(B+B')(C+C') + (A+A')B'C$$

$$= (AB + AB')(C+C') + (A'B'C + A'B'C)$$

$$\rightarrow ABC + ABC' + AB'C + AB'C' + \\ A'B'C + A'B'C.$$

- Number of logical expressions  $= 2^{2^n}$   
 $n \rightarrow \text{no. of variables.}$

## \* Positive & Negative Logic.

### Positive logic.

Higher voltage corresponds to 1.

Lower voltage corresponds to 0.

### Negative logic.

Higher voltage corresponds to 0.

$$\text{Eg. } \begin{cases} \text{logic 0} \rightarrow -5V \\ \text{logic 1} \rightarrow 0V \end{cases} \quad \text{Positive logic.}$$

## \* Dual Form:

- Positive & Negative Logic AND Gate:

A	B	Y	+ve logic	+ve logic
0	0	0	0	1
0	1	0	0	1
1	0	0	0	1
1	1	1	1	0

0 → Low }  
1 → High } +ve logic.

1 → low } -ve  
0 → high } logic

- Positive & Negative Logic OR Gate:

A	B	Y	+ve logic	+ve logic
0	0	0	1	1
0	1	1	1	0
1	0	1	0	1
1	1	1	0	0

$$\left\{ \begin{array}{l} \text{+ve logic AND} \equiv \text{-ve logic OR} \\ \text{+ve logic OR} \equiv \text{-ve logic AND.} \end{array} \right.$$

- Dual form is used to convert between

+ve & -ve logic.

Eg.  $A \cdot B \xrightarrow{\text{Dual}} A + B$ .

$C + D \xrightarrow{\text{Dual}} C \cdot D$ .

Acquire :: https://http://:: proxy "http://12proxy":<port>  
ftp /etc/apt/apt.conf

## \* Self Dual:

For any logical expression, two times dual gives the same expression. In self dual expression, one time dual gives the same expression.

$$\text{Eg. } F = AB\bar{C} + \bar{A}B\bar{C} + ABC.$$

$$F' = (A+B+\bar{C})(\bar{A}+B+C)(A+B+C).$$

$$(F')' = (\bar{A}\bar{B}\bar{C}) + (\bar{A}B\bar{C}) + (AB\bar{C})$$

$$F \equiv (F')'$$

$$\text{Eg. } G = A \cdot B + B \cdot C + A \cdot C \quad \text{Self dual expression.}$$

$$G' = (A+B)(B+C)(A+C).$$

$$= \{B+(A+C)\}(A+C).$$

$$= AB + AAC + BC + ACC.$$

$$= AB + BC + AC.$$

$$G = G' \quad (\text{Self Dual})$$

- For  $n$  variables, there are

$2^{2^{n-1}}$  number self duals.

## \* Complementing:

AND  $\leftrightarrow$  OR

•  $\leftrightarrow$  +

0  $\leftrightarrow$  1


$$\text{Eg. } F = A\bar{B} + \bar{A}B \quad \left. \right\} \text{Using de Morgan's.}$$

$$\bar{F} = A\bar{B} + \bar{A}\bar{B}.$$


$$\text{Eg. } G = ABC + \bar{A}BC + A\bar{B}C.$$

$$\begin{aligned}\bar{G} &= (\overline{ABC + \bar{A}BC + A\bar{B}C}) \\ &= (\overline{ABC} + \overline{\bar{A}BC}) \cdot (\overline{A\bar{B}C}) \\ &= (\overline{ABC}) (\overline{\bar{A}BC}) (\overline{A\bar{B}C})\end{aligned}$$

\* Venn Diagram.

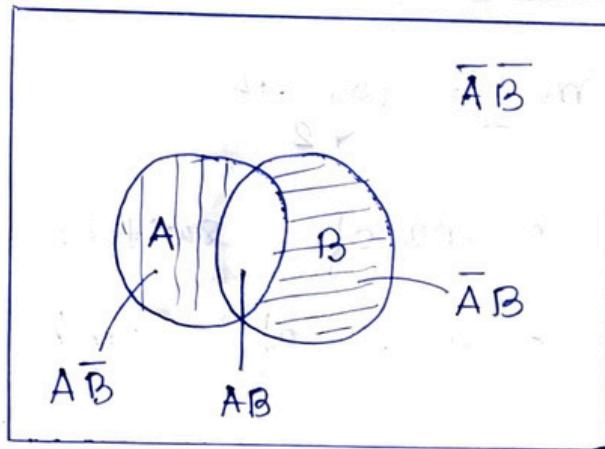

Eg.

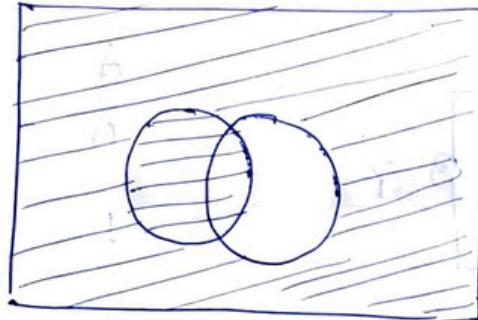

Minimise the SOP expression for shaded region.


$$Y = \bar{A}\bar{B} + A\bar{B} + AB$$

$$= (A + \bar{A})\bar{B} + AB$$

$$= \bar{B} + AB$$

$$= A + \bar{B}$$

Eg.

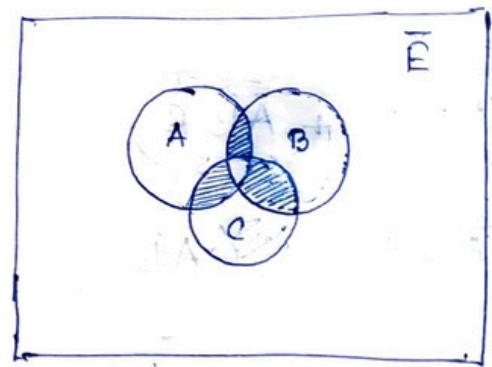

$$F = (AB\bar{C} + \bar{A}BC + A\bar{B}C).$$


## \* Switching Circuits.:

$$\bullet m = \log_2 n$$

$m \rightarrow$  no. of switches required


$n \rightarrow$  no. of combinations.

### Series Switch. (A)

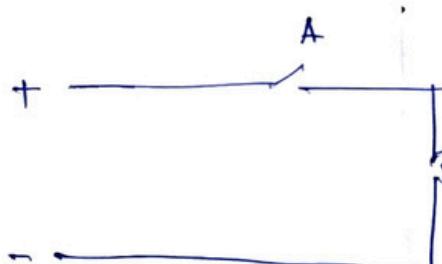


A	Y
0	0
1	1

### Parallel Switch. (NOT)

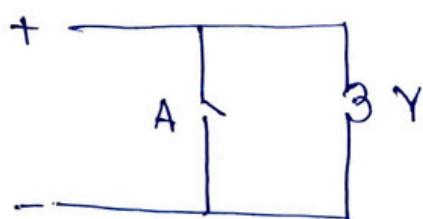



A	Y
0	1
1	0

### AND

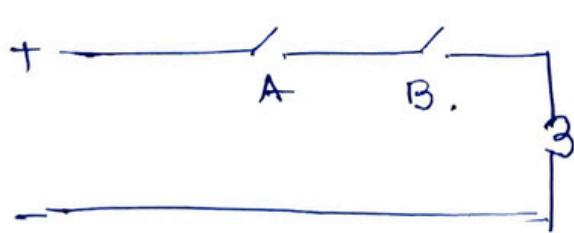

### OR

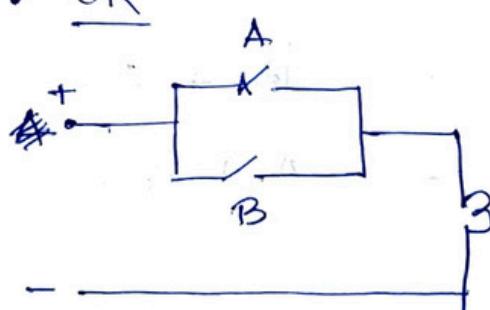



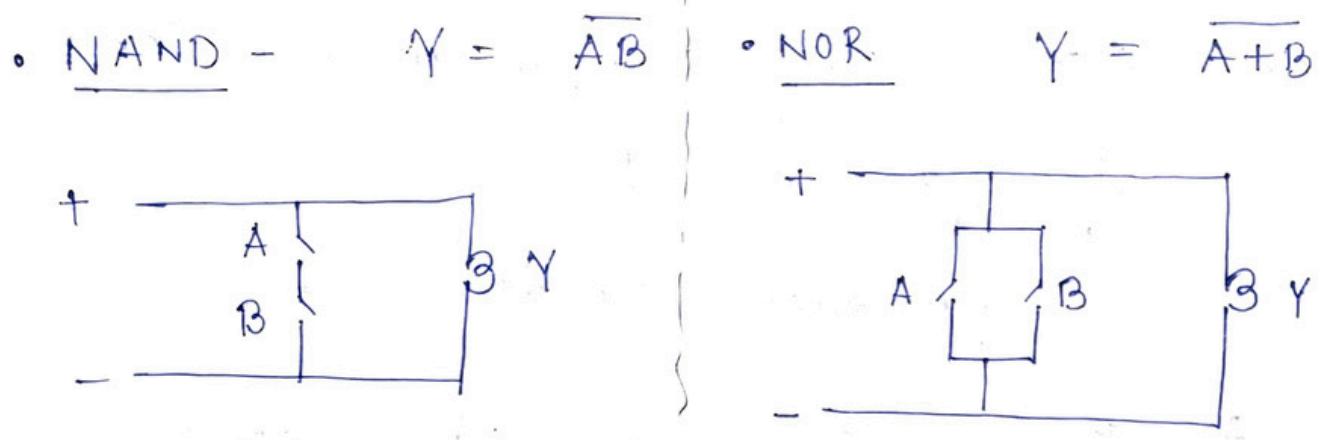


• XOR  $Y = AB' + A'B$

$\oplus$   $= A \oplus B$

• XNOR  $Y = AB + A'B'$

$\odot$   $= A \odot B$

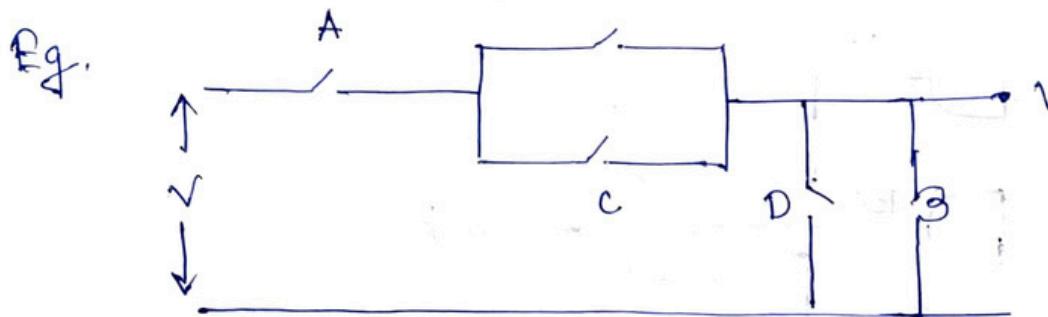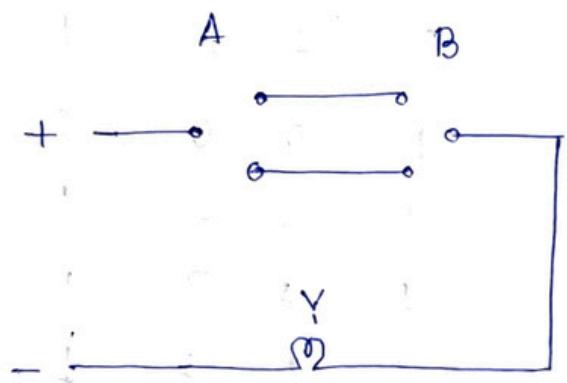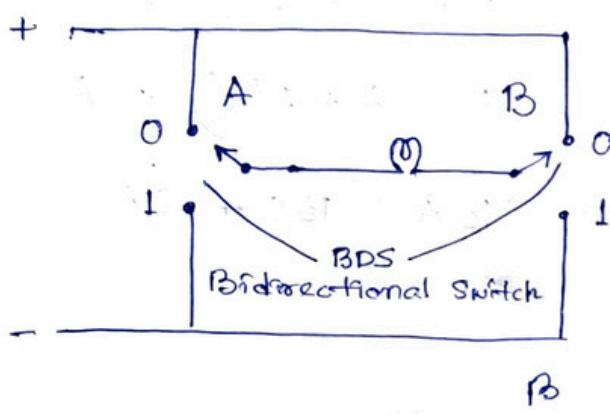

$$Y = A(B+C)\bar{D}$$

(Intuitive).

$$Y = A\bar{B}\bar{D} + AC\bar{D}$$

$$= A(B+C)\bar{D}$$

find ways to glow the bulb of OR them, then simplify.

## \* Statement Problems.

- Bq. High when i) B, C true ii) A, C false  
 iii) A, B, C true iv) A, B, C false.

$$Y = BC + A'C' + ABC + A'B'C'$$


$$= BC + A'C'$$

Eg. A, B, C i/p. O/p high when majority of i/p are 1.

Implement circuit.



A	B	C	F	$F = A'B'C + AB'C + ABC' + ABC$
0	0	0	0	
0	0	1	0	
0	1	0	0	$= A'B'C + AB'C + AB$
0	1	1	1	$= A'B'C + A(B+C)$
1	0	0	0	$= A'BC + AB + AC$
1	0	1	1	$= B(A+A'C) + AC$
1	1	0	1	$= BA + BC + CA$
1	1	1	1	

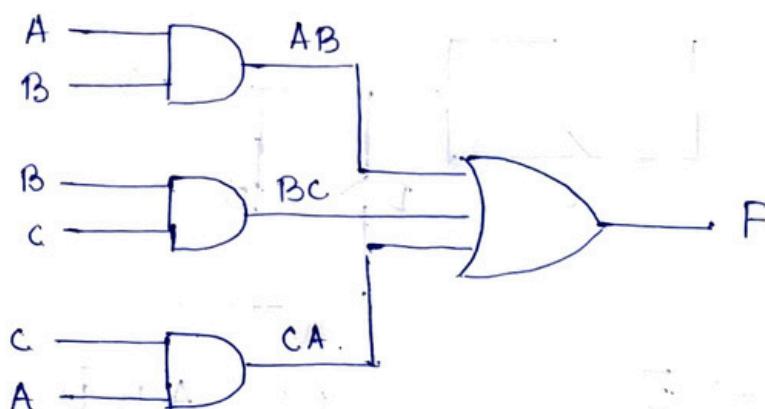

## \* Number Systems

Defines a set of values used to represent quantity.

Name	Base/ Radix ( $r$ )	(No. of distinct digits)
Binary	2	[0, 1] Bits
Octal	8	
Decimal	10	Digits -
Duodecimal	12	$(0, \dots, r-1)$
Hexadecimal	16	

## \* Binary Number System : $(101)_2 \approx (5)_{10}$

- Bits = 0 & 1.

- Any number system → decimal

ABCDE

$$\rightarrow A \times r^4 + B \times r^3 + C \times r^2 + D \times r^1 + E \times r^0$$

AB.CD

$$\rightarrow A \times r^3 + B \times r^2 + C \times r^{-1} + D \times r^{-2}$$

- MSB (Most Significant Bit)

10101  
MSB

- LSB (Least Significant Bit)

10101 LSB.

- 1 Nibble = 4 bits      BCD → Hex

1 Byte = 8 bits

1 Word = 16 bits = 2 bytes.

1 double word = 32 bits = 4 bytes

- Decimal → Binary.

Divide integer part by  $r$ , base  
and multiply fractional part by  $r$ .

Eg.  $(13)_{10} = (1101)_2$

Divisor	Dividend	Rem.
2	13	1
2	6	0 ↑
2	3	1
2	1	1
	0	

Eg.  $(25.625)_{10} \equiv 11001.101$

$$\begin{array}{r}
 0.625 \times 2 = 1.25 \\
 0.25 \times 2 = 0.50 \\
 0.50 \times 2 = 1.00
 \end{array}
 \quad
 \begin{array}{r}
 2 \quad 25 \quad 1 \\
 2 \quad 12 \quad 0 \\
 2 \quad 6 \quad 0 \\
 2 \quad 3 \quad 1 \\
 2 \quad 1 \quad 1 \\
 0
 \end{array}$$

\* Decimal  $\rightarrow$  Octal

Eg.  $(112)_{10} \rightarrow (160)_8$

$$\begin{array}{r}
 112 \\
 8 \quad 14 \quad 0 \\
 8 \quad 1 \quad 1 \\
 0
 \end{array}$$

(Free from finding remainder)

Eg.  $(25.625)_{10} \rightarrow (31.5)_8$

$$\begin{array}{r}
 0.625 \times 8 = 5.000 \\
 8 \quad 3 \quad 3 \\
 0
 \end{array}$$

\* Decimal  $\rightarrow$  Hexadecimal

Eg.  $(254)_{10} \rightarrow (FE)_{16}$

$$\begin{array}{r}
 254 \\
 16 \quad 15 \quad 14 \quad E
 \end{array}$$

Eg.  $(25.625)_{10} \rightarrow 19.A$

$$\begin{array}{r}
 0.625 \times 16 = 10.00 \\
 A \quad 16 \quad 1 \quad 1 \\
 0
 \end{array}$$

## \* Binary to Decimal.

Generally

$$(a_3 a_2 a_1 a_0 \cdot a_{-1} a_{-2})_r \rightarrow$$

$$a_3 r^3 + a_2 r^2 + a_1 r^1 + a_0 r^0 + a_{-1} r^{-1} + a_{-2} r^{-2}$$

Eg.  $(10101.11)_2 \rightarrow$

$$1 \times 2^4 + 0 + 1 \times 2^2 + 0 + 1 \times 2^0 + 1 \times 2^{-1} + 1 \times 2^{-2}$$

$$= 16 + 0 + 1 + 0.5 + 0.25$$

$$= \cancel{21.75}_{10}$$

## \* Octal to Decimal.

Eg.  $(57.4)_8 \rightarrow$

$$5 \times 8^1 + 7 \times 8^0 + 4 \times 8^{-1}$$

$$= 40 + 7 + 0.5$$

$$= (47.5)_{10}$$

## \* Hexadecimal to Decimal.

Eg.  $(BAD)_{16} \rightarrow$

$$11 \times 16^2 + 10 \times 16^1 + 13 \times 16^0$$

$$= 2989.$$

\* Octal NS. (3 bit bin)

0 000

Octal  $\rightarrow$  Bin.

1 001

$(34 \cdot 75)_8 \rightarrow$

2 010

$(011100 \cdot 111101)_2$ ,

3 011

Bin  $\rightarrow$  Octal

4 100

$(10110 \cdot 11)_2 \rightarrow (010110 \cdot 110)_2$

5 101

6 110

7 111

$\rightarrow (26 \cdot 6)_8$ .

Make group of 3 bits.

\* Hexadecimal NS. (4 bit bin)

0 0000

Hex  $\rightarrow$  Bin

1 0001

2 0010

$(259A)_{16} \rightarrow$

3 0011

$(0010010110011010)_2$

4 0100

5 0101

6 0110

Bin  $\rightarrow$  Hex

7 0111

$(10001001.11)_2 \rightarrow (89.C)_{16}$

8 1000

9 1001

Make group of 4 bits.

A 10 1010

B 11 1011

C 12 1100

D 13 1101

E 14 1110

F 15 1111.

\* Hex  $\rightarrow$  Oct  
Oct  $\rightarrow$  Hex

Eg. (CAD)<sub>16</sub>  $\xrightarrow{\text{Bin}}$   
 $(110010101101)_2$   
 $\xrightarrow{\text{Oct}}$  (6255)<sub>8</sub>.

Eg. (652)<sub>8</sub>  $\xrightarrow{\text{bin}}$  (1AA)<sub>16</sub>  
 $(110101010)_2$

\* Binary Addition.

Eg.  $\begin{array}{r} 110 \\ \times 101 \\ \hline 1011 \end{array}$       Sum      Carry

0 + 0	1	0
1 + 0	1	0
0 + 1	1	6
1 + 1	0	1

\* Binary Subtraction.

Eg.  $\begin{array}{r} 11011 \\ - 10110 \\ \hline 00101 \end{array}$       borrow 2

\* Bin Multiplication.

1010	Product
x 101	
<hr/>	
1010	0 x 0 = 0
	1 x 0 / 0 x 1 = 0
	1 x 1 = 1
6000	
1010	
<hr/>	
100010	

$$\begin{array}{r}
 1010 \\
 \times 11 \\
 \hline
 1010 \\
 1010 \\
 \hline
 1110
 \end{array}
 \quad
 \begin{array}{r}
 * \text{Binary Division.} \\
 \hline
 111 \\
 110 \overline{)101010} \\
 110 \\
 \hline
 101 \\
 110 \\
 \hline
 0110
 \end{array}$$

\* Complements.

1.  $r$ 's Complement (Radix Complement).

$r$ 's complement  $\rightarrow r^n - N$

$r$  - base,  $n$  - no. of digits.

$N$  - given number

Eg.  $N = 5690$ .

$$\begin{aligned}
 10\text{'s complement} &= 10^4 - 5690 \\
 &= 4310.
 \end{aligned}$$

Eg.  $N = 1101$

$$\begin{aligned}
 2\text{'s complement} &= 2^4 - 1101 \\
 &= (16)_{10} - 1101 \\
 &= 10000 - 1101 \\
 &= 0111
 \end{aligned}$$

2.  $(r-1)$ 's complement (Diminished radix complement).

$$(r-1)\text{'s comp.} = r^n - N - 1.$$

No borrow operation is involved.

$$= r\text{'s comp.} - 1.$$

Eg. 7's comp. of  $(5674)_8$

$$= 8^4 - 5674 - 1.$$

$$= (4096)_{10} - 5671 - 1$$

$$\begin{array}{r} 7777 \\ - 5674 \\ \hline 2103 \end{array}$$

$$= 10000 - 5674 - 1$$

$$= 7777 - 5674$$

$$= 2103$$

Eg. 8's comp. of  $(5674)_8$

$$= 2103 + 1$$

$$= 2104.$$

Eg. 1's complement of 1101.

$$\begin{array}{r} 1111 \\ - 1101 \\ \hline 0010 \end{array} \rightarrow \text{Ans}$$

2's comp. =  $0010 + 1$   
 $= 0011.$

Eg. 1's complement of  $(1010)_2$ .


$$\begin{array}{r} 1111 \\ - 1010 \\ \hline 0101 \end{array} \rightarrow \text{Ans.}$$

② Shortcut for 2's complement:


Write given number → starting from LSB

copy all zeroes till first 1 →

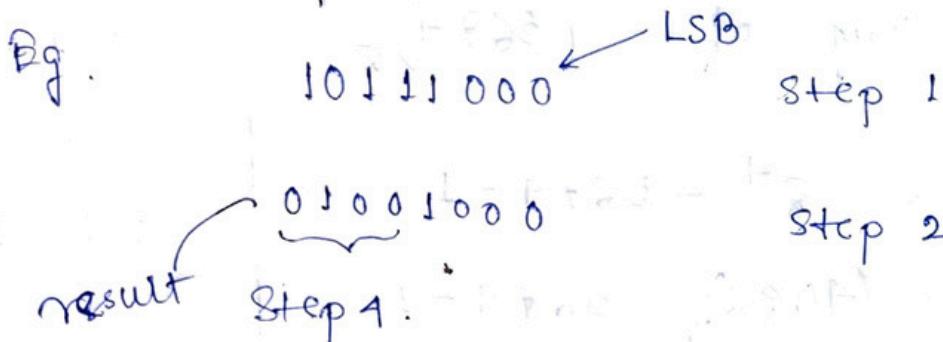Copy first 1 → Complement all remaining bits.



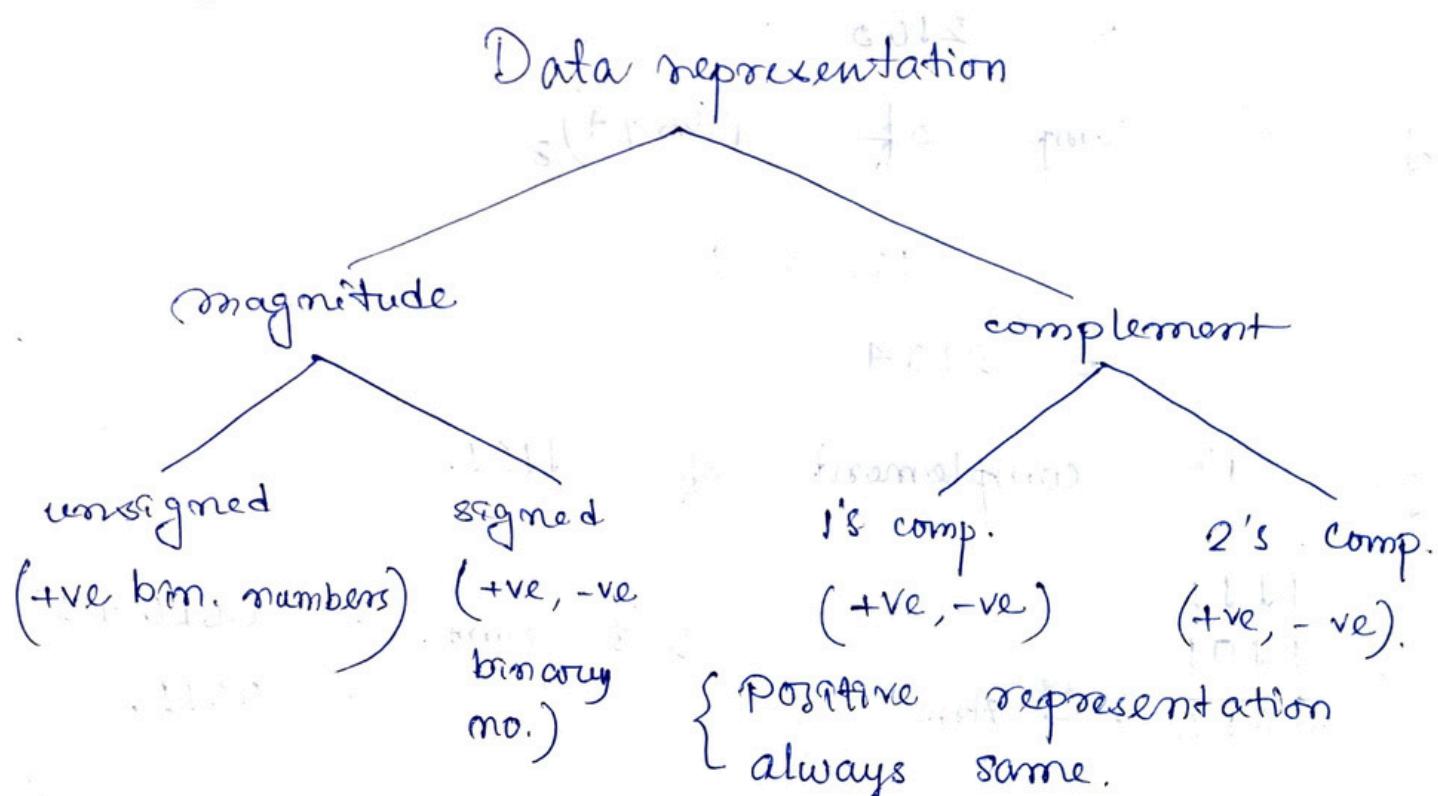\* Data Representation using Signed Magnitude:



• Unsigned

$$110 \rightarrow +6$$


$$-6 \rightarrow \text{can't represent}$$

• Signed

$$+6 \rightarrow 0110$$

$$-6 \rightarrow 1110$$

Sign bit (MSB)

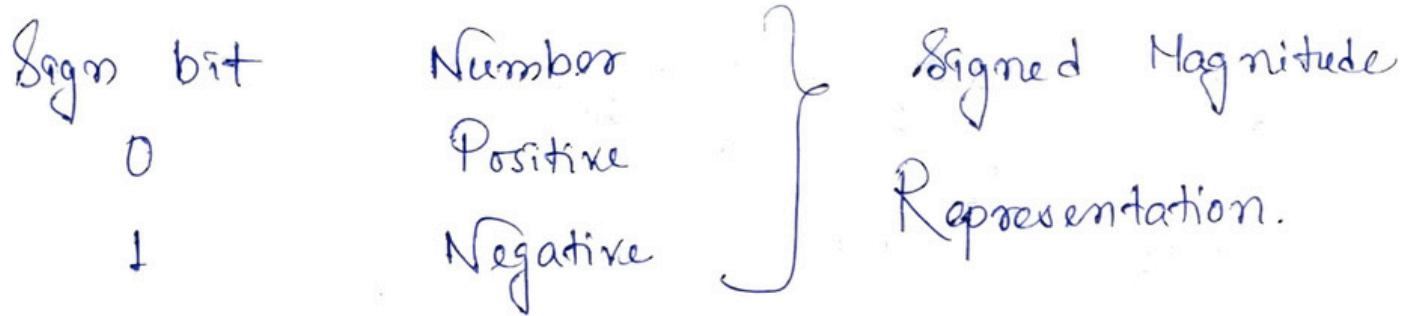

• Range  $- (2^{n-1} - 1)$  to  $+ (2^{n-1} - 1)$   
 (Signed Magnitude)       $n \rightarrow$  no. of variables

• I's complement.

$$\begin{array}{rcl}
 +6 & = & 0110 \\
 -6 & = & 1001
 \end{array}
 \quad \text{I's complement.}$$

$$+0 = 0000 \text{ (+ve zero)}$$

$$-0 = 1111 \text{ (-ve zero)}$$

Range.  $- (2^{n-1} - 1)$  to

$(2^{n-1} - 1)$ .

• 2's complement.

$$\begin{array}{rcl}
 +6 & = & 0110 \\
 -6 & = & 1001 \\
 & & \downarrow +1 \\
 & & 1010
 \end{array}
 \quad \begin{array}{l}
 \text{1's} \\
 \text{2's}
 \end{array}
 \quad \begin{array}{l}
 \text{Range.} \\
 -2^{n-1} \text{ to} \\
 (2^{n-1} - 1)
 \end{array}$$


• MSB indicates sign.

④ Barn. Subtraction using I's comp. :

i) Convert no. to be subtracted to its I's comp. form.

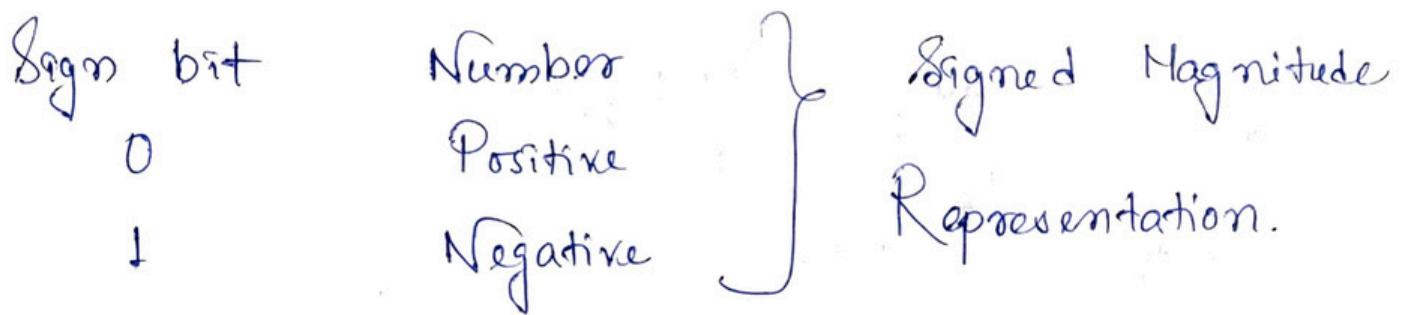ii) Perform addition.

\*\*\* iii) If final carry is 1, then add it to the result. If 0, result is negative & in the I's complement form.



- Range -  $(2^{n-1} - 1)$  to  $+ (2^{n-1} - 1)$   
 (Signed Magnitude)       $n \rightarrow$  no. of variables

- 1's complement.

$$\begin{array}{rcl} +6 & = & 0110 \\ -6 & = & 1001 \end{array} \quad \text{1's complement.}$$

$$\begin{array}{l} +0 = 0000 \text{ (+ve zero)} \\ -0 = 1111 \text{ (-ve zero)} \end{array} \quad \begin{array}{l} \text{Range.} - (2^{n-1} - 1) \text{ to} \\ (2^{n-1} - 1). \end{array}$$

- 2's complement.

$$\begin{array}{rcl} +6 & = & 0110 \\ -6 & = & 1001 \end{array} \quad \begin{array}{l} \text{1's} \\ \text{2's} \end{array} \quad \begin{array}{l} \text{Range.} - 2^{n-1} \text{ to} \\ (2^{n-1} - 1) \end{array}$$

- MSB indicates sign.

\* Barn. Subtraction using 1's comp. :

- Convert no. to be subtracted to its 1's comp. form.
- Perform addition.
- If final carry is 1, then add it to the result. If 0, result is negative & in the 1's complement form.

$$\text{Eg: } (1100)_2 - (0101)_2$$

A              B

$$-B = 1010$$

$$A + (-B) = 1100 + 1010 = 10110$$

$$0110 + 1 = 0111 \quad (\text{Ans})$$

$$\text{Eg. } (0101)_2 - (1100)_2$$

A              B

$$-B = 0011$$

$$A + (-B) = 0101 + 0011 = 01000$$

↓  
-ve.

1's comp.

$$A + (-B) = 0111 (1's \text{ comp. of } 0011) + 0000 = 0111$$

\* Pm. Subtraction using 2's comp.:

- Find 2's comp. of the number to be subtracted.
- Perform addition.
- If final carry is generated then the result is true & in true form. If not generated, then it is available in 2's complement form.

$$\text{Eg. } -(0100)_2 + (1001)_2$$

B              A

$$-B = 1100$$

$$1001 + 1100 = 10101$$

Result is 0101.

$$\text{Eg. } (0110)_2 - (1011)_2$$

$$\begin{array}{r} A \\ - B \\ \hline = 0101 \end{array}$$

$$0110 + 0101 = 1011$$

$$\begin{array}{r} 2^8 \\ 0101 \\ \leftarrow 0100 \\ + 1 \end{array}$$

\* Condition for Overflow?

x & y are sign bits of two numbers

z, first sign bit of result

$$\begin{array}{ll} \bar{x}\bar{y}z + xy\bar{z} = 0 & (\text{No overflow}) \\ & \\ & = 1 & (\text{Overflow}). \end{array}$$

\* Codes. (group of symbols).

Classification —

Weighted  
(Primary,  
2421,  
8421)

Non-weighted  
(xs-3, gray)

Reflective  
code/  
self-comple-  
menting

(2421, xs-3)

Sequential  
(8421,  
xs-3)

Alpha-  
numeric  
(ASCII)

Error  
detecting  
& correcting  
codes.

(Hamming  
code).

## \* Binary Coded Decimal (BCD Code) :

- Each decimal digit is represented by a 4-bit binary number.
- Positional weights → 8 4 2 1
- Also called 8421 code.

Decimal	BCD
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

Decimal No. → BCD.

$$i) (17)_{10} \rightarrow (00010111)$$

BCD → Decimal No.

$$ii) (10100) \rightarrow (14)_{10}$$

$$\xleftarrow{\quad} \xrightarrow{\quad} (00010100)$$

- Packed BCD - BCD representation for dec. No.  $> 9$ .

- BCD is less efficient than Binary as it uses more no. of bits.

### BCD Addition.

1. Sum  $\leq 9$ , Final carry = 0      Correct ans.

2. Sum  $\leq 9$ , " " " = 1      Add (0110) to ans.

3. Sum  $> 9$ , " " " = 0      Add (0110) to ans.

Eg.  $(2)_{10} + (6)_{10}$

$$\begin{array}{r} 0010 \\ + 0110 \\ \hline \end{array}$$

$$= \underline{\underline{(Ans)}}$$

Sum  $< 9$ , FC = 0.

$$\text{Eg. } (3)_{10} + (7)_{10}$$

$$\downarrow \quad \downarrow$$

$$0011 \quad 010111$$

$$= \begin{array}{r} 1010 \\ \downarrow + 0110 \\ \text{Sum} \end{array} > 9.$$

$$\begin{array}{r} 000 \\ | 10000 \\ \downarrow \\ (10)_{10} \end{array} \text{ BCD}$$

$$\text{Eg. } (8)_{10} + (9)_{10}$$

$$\downarrow \quad \downarrow$$

$$1000 \quad 1001$$

$$= \begin{array}{r} 1001 \\ \downarrow \text{ Sum} < 9 \\ \text{FC} \end{array}$$

$$\downarrow + 0110$$

$$\begin{array}{r} 10111 \\ \downarrow \\ (17)_{10} \end{array} \text{ BCD}$$

$$\text{Eg. } (57)_{10} + (26)_{10}$$

$$\begin{array}{r} \downarrow \quad \downarrow \\ 01010111 \quad 00100110 \end{array}$$

$$= \begin{array}{r} 01111001 \\ 7 < 9 \quad \frac{13}{13} > 9 \end{array}$$

$$\begin{array}{r} 01111101 \\ + 01111101 \\ \hline 10000011 \end{array} \text{ BCD}$$

Check every 4 bits  
 individually & perform it  
 & check conditions

$$\downarrow$$

$$(83)_{10}$$

\* Shift ADD-3 Method. (Parn.  $\rightarrow$  BCD).

Operations	Tens	Ones	Decimal	$(15)_{10}$
Original No.			1111	
Shift		1	111	
Shift		11	11	
Shift		111	1	
Add-3		+ 011	1	
Shift		<u>10101</u>	BCD for 15.	

* 2421 Code (BCD.)	Self - Complementing
Decimal Digit	Set I      Set II $\begin{array}{r} 2^4 \ 2^3 \ 2^2 \ 2^1 \\ \hline \end{array}$ $\begin{array}{r} 2^4 \ 2^3 \ 2^2 \ 2^1 \\ \hline \end{array}$ (Complement)

0	0 0 0 0	0 0 0 0
1	0 0 0 1	0 0 0 1
2	0 0 1 0	0 0 1 0
3	0 0 1 1	0 0 1 1
4	0 1 0 0	0 1 0 0
5	0 1 0 1	0 1 1 1
6	0 1 1 0	1 1 0 0
7	0 1 1 1	1 1 0 1
→ 8	1 1 1 0	1 1 1 0
→ 9	1 1 1 1	1 1 1 1

\* Excess-3 Code. ( $\times 3$ ) Self - Complementing.

• Decimal  $\rightarrow$  8-4-2-1  $\xrightarrow{\text{Add } 0011}$  Excess-3  
(BCD) (3)

Eg. 5  $\rightarrow$  0101  $\xrightarrow{+0011}$  1000

• Unweighted Code., 4-bit Code

• Decimal      BCD       $\times 3$

0	0000	+ 0011	0011
1	0001		0100
2	0010		0101
3	0011		0110
4	0100		0111
5	0101		1000
6	0110		1001
7	0111		1010
8	1000		1011
9	1001		1100

$$\text{Eg. } (24)_{10} \rightarrow (\overset{\text{BCD}}{00100100}) \xrightarrow{\text{Add}} \begin{array}{r} 00100100 \\ + 00110011 \\ \hline \boxed{01010111} \end{array}$$

Ans.

$$\text{Eg. } (658)_{10} \rightarrow (\overset{\text{BCD}}{0110\ 0101\ 1000})$$

$\downarrow + 0011$

$\boxed{1001\ 1000\ 1011}$

- XS-3 is only unweighted code that is self-complementing.

\* Whether self complementing or not -

Weights. —  $w_1, w_2, w_3, w_4$ .

[For weighted codes]

$$w_1 + w_2 + w_3 + w_4 = 9 \sim \text{Self Complementing}$$

$$\neq 9 \sim \text{Not m n}$$

\* Excess-3 Code Addition:

$$\text{Eg. } (2)_{10} + (5)_{10}$$

$\downarrow \quad \downarrow$

BCD    0010    0101

$\downarrow \quad \downarrow$

XS3    + 0011    0101    1000

$0101 \xrightarrow{\text{XS3}}$   
 $+ 1000 \xrightarrow{\text{XS3}}$   
 $\hline 1101 \xrightarrow{\text{XS6}}$   
 $- 0011 \quad \text{Subtract 3,}$   
 $\hline 1010 \quad \text{(Ans)}$

\*\* Eg.  $(27)_{10} + (39)_{10}$

$\downarrow \quad \downarrow$

BCD    00100111    00111001

$\downarrow 0011 \quad \downarrow$

XS3    01011010    01101100

$+ 0011$

$0101 \xrightarrow{\text{FC=1, add 3}}$   
 $+ 0110 \xrightarrow{\text{FC=0, sub. 3}}$   
 $\hline 11000110$   
 $- 0011 + 0011$   
 $\hline 10011001 \quad \text{Ans.}$

## \* Gray Code ( Frank Gray, AT&T ).

- Reflected binary code (RBC).
- Unweighted, cyclic code.
- Unit distance code & minimum error code.
- Two successive values differ in only one bit.
- Binary no. converted to GC to reduce switching operation.

Decimal

Binary

GC

0

0000

0000

2

0001

0001

3

0011

0010

4

0100

0110

5

0101

0111

6

0110

0101

7

0111

0100

8

1000

1100

9

1001

1101

10

1010

1111

11

1011

1110

12

1100

1010

13

1101

1011

14

1110

1001

15

1111

1000

16

10000

0000

- Binary  $\rightarrow$  GC. (MSB remains same)

Step 1. Record MSB as it is.

Step 2. Add MSB to the next bit, record the sum, neglect carry

Step 3. Repeat the process.

)  
(XOR)

Eg.  $(1011)_{\text{Bin}}$

$$\begin{array}{r}
 1011 \\
 + 1010 \\
 \hline
 1110 \quad \text{Ans.}
 \end{array}$$

Eg.  $(1110)_{\text{Bin}}$

$$\begin{array}{r}
 1110 \\
 + 1001 \\
 \hline
 1001 \quad \text{Ans.}
 \end{array}$$

- GC  $\rightarrow$  Binary.

Step 1. Record MSB as it is.

Step 2. Add MSB to next bit of Gray code, record sum & neglect carry (X-OR)

Step 3. Repeat.

Eg.  $(1110)_{\text{gc}}$

$$\begin{array}{r}
 1110 \\
 + 1011 \\
 \hline
 1011 \quad (\text{Ans})
 \end{array}$$

Eg.  $(1001)_{\text{gc}}$

$$\begin{array}{r}
 1001 \\
 + 1110 \\
 \hline
 1110 \quad (\text{Ans})
 \end{array}$$

## \* Parity:

→ Single bit error is detected by it.

→ i) Even parity - No. of Is even

ii) Odd parity → No. of 1's odd.

010011 , 010010

1100 0 1100 1

Transmit                      Receive .

Even parity

Due to  
noise

10501; 1

Odd x

Error detected.

\* Hamming Code → Error Detection.

→ Given by R.W. Hamming


→ Easy to implement

→ 7-bit hamming code is used commonly.

→ Data bits = 4 for 7-bit

Parity bits - 3

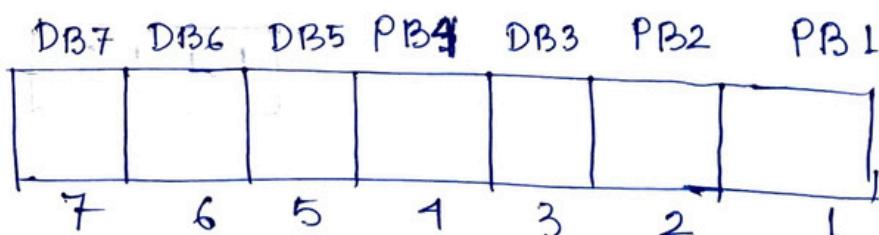→ Position of parity bits  $\rightarrow 2^n$ .



PB ↓ associated with DB3, DB5, DB7

PB2            m            m            DB3, DB6, DB7

PB2 n m DB5, DB6, DB7

Eg. (1011) Transmitter side

1	0	1	0	1	0	1
$d_7$	$d_6$	$d_5$	$P_1$	$d_3$	$P_2$	$P_1$

$P_1 \rightarrow d_3, d_5, d_7 \rightarrow [1] 1 1 1$  even parity

$P_2 \rightarrow [0] 1 0 1$   $P_3 \rightarrow [0] 1 0 1$

Error detection -

due to noise  $\rightarrow$

$d_7 d_6 d_5$   
1 1 1  
 $d_3$   
0 1 0 1.  
 $P_1$   $P_2$   $P_3$

Check  $P_1 \rightarrow d_3, d_5, d_7$   
even parity ✓

Check  $P_2 \rightarrow d_3, d_6, d_7$   
X error

Check  $P_3 \rightarrow d_5, d_6, d_7$   
X error.

### \* Hamming Code - Error Correction

Eg. If the 7 bit hamming code word received by a receiver is 1011011, assuming the even parity state. whether the received code is correct or wrong? Locate error bit. [Correct - 1001011]

$$\rightarrow P_1 \rightarrow 1 \quad (110) \times P_1 = 1$$

$d_7$	$d_6$	$d_5$	$P_1$	$d_3$	$P_2$	$P_1$
1	0	1	1	0	1	1

$$P_2 \rightarrow 1 \quad (100) \vee P_2 = 0$$

$$P_4 \rightarrow 1 \quad (101) \times P_4 = 1$$


$$(P_1 P_2 P_3) = (101)_2 \equiv (5)_{10} \text{ error}$$

Error bit



Whenever parity unmatches  
 $P_i = 1$ ; otherwise  
 $P_i = 0$ .
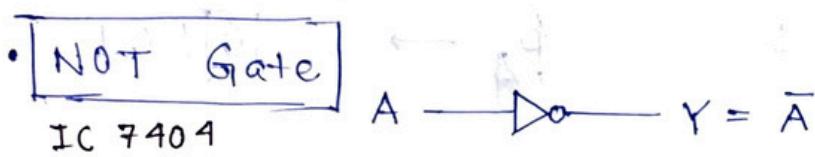
## \* Logic Gates.

- A physical device that performs logic operation on one or more logical inputs, and produces a single logical output.
- Gates - i) basic (NOT, AND, OR)  
ii) universal (NAND, NOR)  
iii) arithmetic ( $x$ -OR,  $x$ -NOR)



A	Y
1	0
0	1

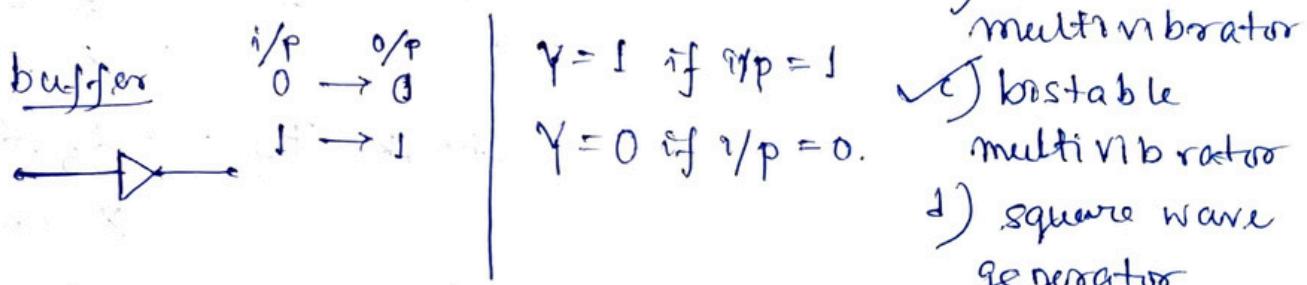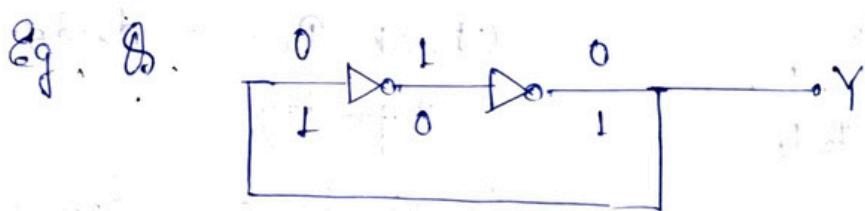

a) Not a buffer because of the feedback.

astable not stable in either state; continually changes from one state to another.


b) Not astable.

c) bistable stable in either state.

flipped by an external trigger pulse.

d) Not square wave generator.


Eg.

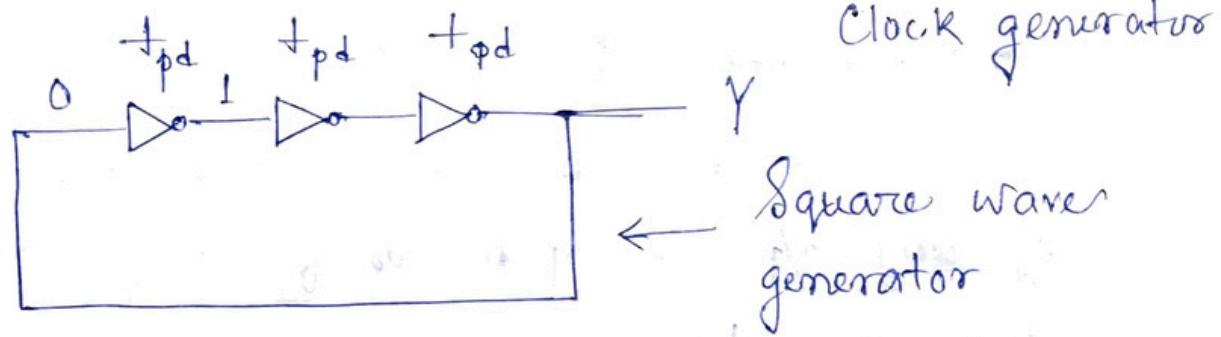

$t_{pd}$  → propagation delay for each NOT gate

{ Astable MV.  
Ring Oscillator }


graph -

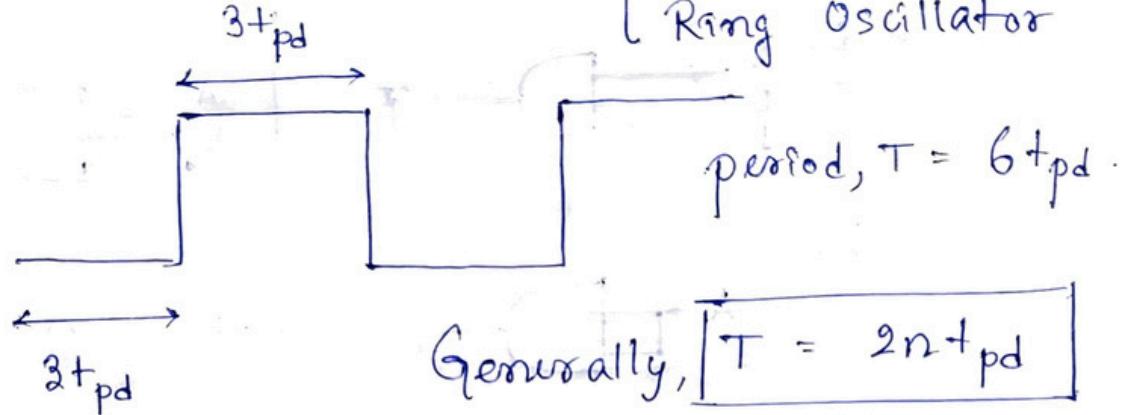

$m \rightarrow$  no. of NOT gates.

• AND Gate o/p high when all i/p high.

IC 7408

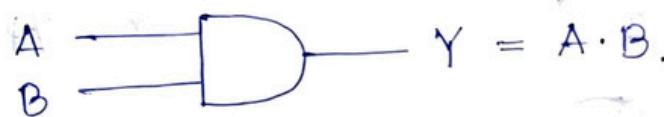

$$\rightarrow A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

[Associativity]

$$\rightarrow A \cdot B = B \cdot A$$

[Commutativity]

Enable & Disable.

→ When  $A = 0$ ,  $Y = 0$ .

0 is disable for AND Gate.

→ When  $A = 1$ ,  $Y = 0/1$


1 is enable (buffer).

## Unused I/P.


→ In TTL logic (Transistor-Transistor) if any I/P is open or floating it will act as 1.

→ In ECL logic if open, act as 0.

→ i)

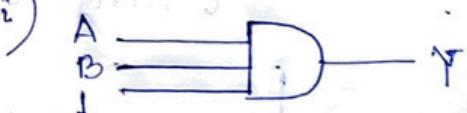

N<sub>CC</sub>

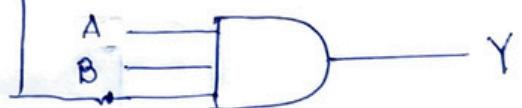

ii)

$$Y = A \cdot A' = A$$

iii)

$$Y = A \cdot 1 \quad \text{TTL logic}$$

**OR Gate**

One of all or all are high.

IC 7432

→ Out high


$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

$$(A+B)+C = A+(B+C)$$

$$A+B = B+A$$

→ Enable & Disable.

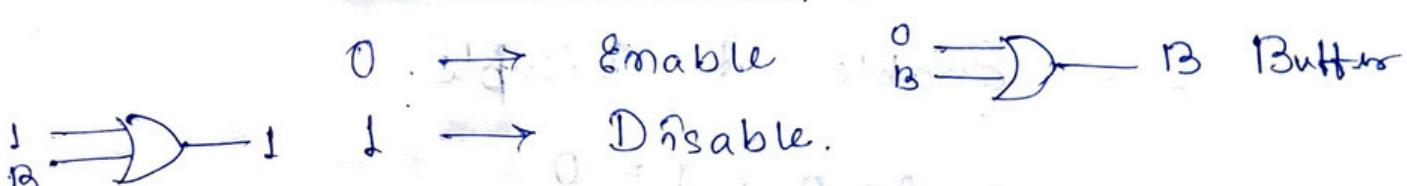

→ Unused I/P

TTL - 1

ECL - 0.

i) Connect to 0 V

$$Y = A + 0 = A$$

ii)


$$Y = A + B + B \\ = A + B$$

iii) ECL logic




$$Y = A + 0 = A$$

floating

Eg.

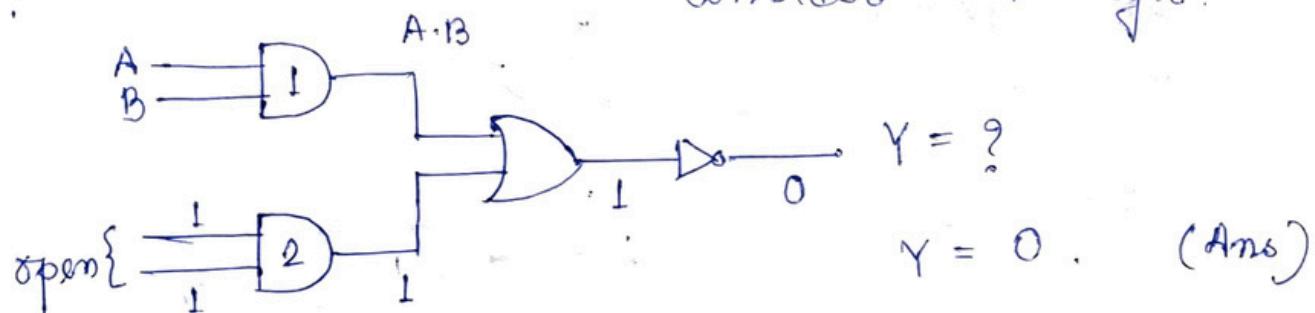

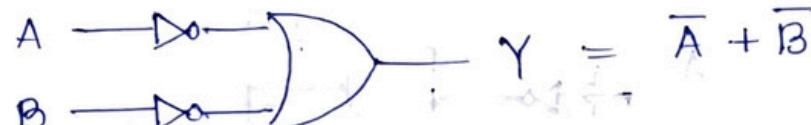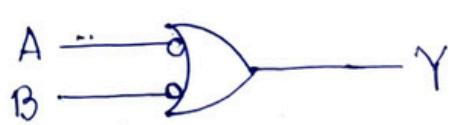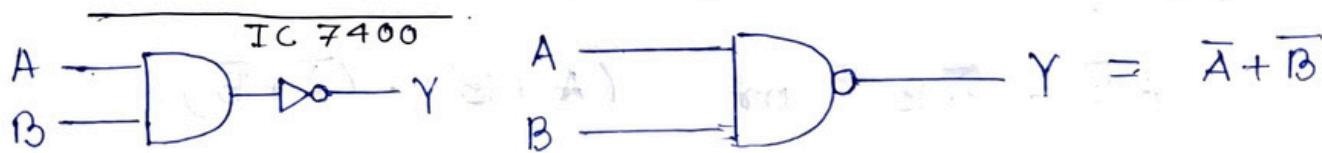\* NAND Gate.  $(\overline{A} + \overline{B})$  Bubbled OR



0 → disable




1 → enable

Unused i/p - same as AND.

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

\* NOR Gate  $(\overline{A} \cdot \overline{B})$  Bubbled AND.

IC 7402

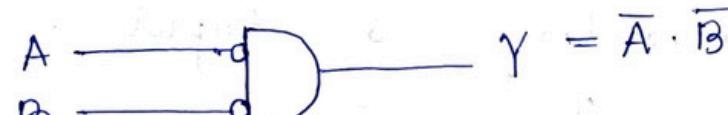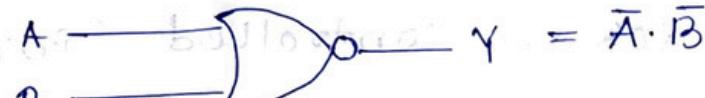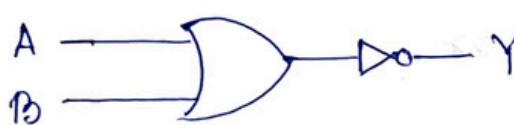

0 → enable

1 → disable.

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


Unused i/p - same as OR

\* XOR Gate.

IC 7486




IEEE Symbol -

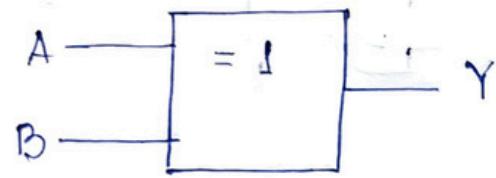

$$Y = A \oplus B$$

$$= AB + \bar{A}B \quad \text{or} \quad (A+B) \cdot (\bar{A}+\bar{B})$$

Ckt

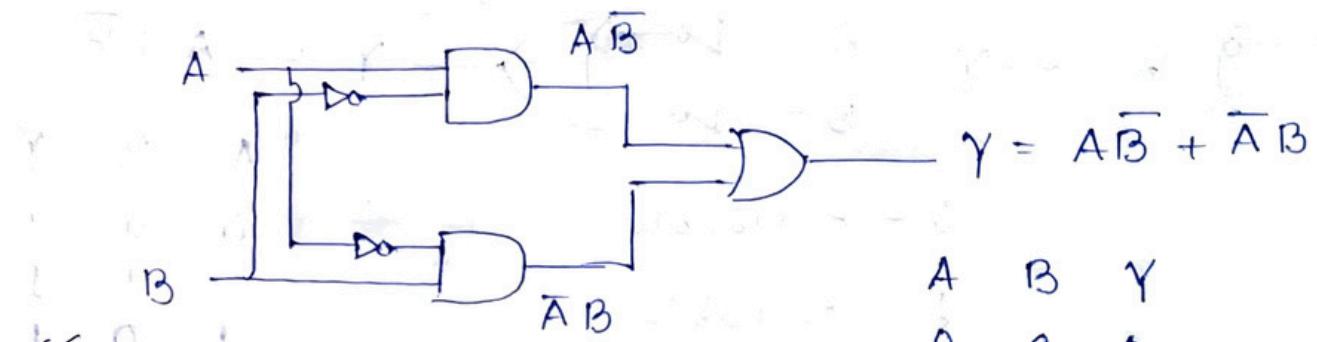



✓ Enable - 0 buffer  
Enable - 1 inverter

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

- XOR is odd one's detector.

- XOR — controlled inverter

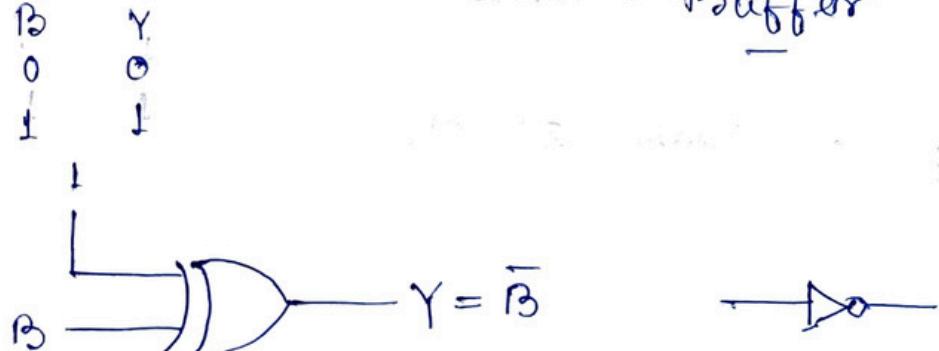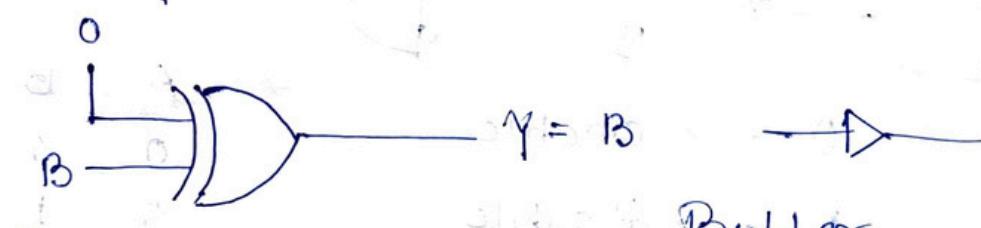We can make it buffer or inverter according to input.



Inverter -

B	Y
0	1
1	0

## \* Properties of XOR :

$$1. A \oplus A = 0$$

$$A \oplus \bar{A} = 1$$

$$A \oplus 0 = A$$

$$A \oplus 1 = \bar{A}$$

$$3. A \oplus A \oplus A = A$$

$A \oplus A \oplus \dots \oplus \dots n \text{ times} =$

$A, n \rightarrow \text{odd}$

$0, n \rightarrow \text{even.}$


2. If  $A \oplus B = C$  then

$$B \oplus C = A$$

$$A \oplus C = B$$

$$A \oplus B \oplus C = 0.$$

Eg.

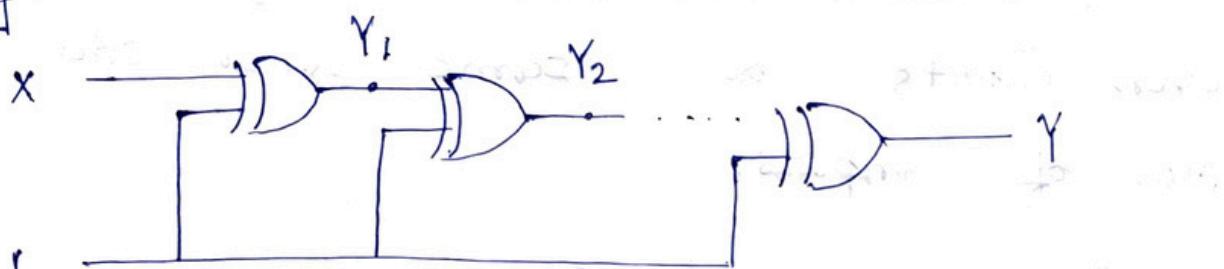

Cascading of 20 XOR Gates.


$$Y_1 = X \oplus I = \bar{X}$$

$$Y_2 = \bar{X} \oplus I = X$$


$$\vdots \\ Y_{20} \Rightarrow Y = X.$$

## \* XNOR Gate (A ⊙ B)

$$AB + \bar{A}\bar{B}$$

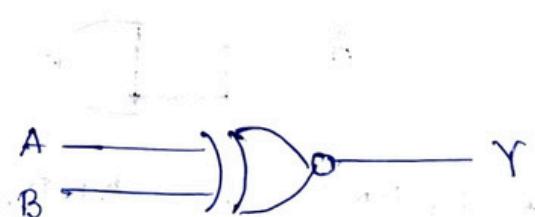

IEEE Symbol

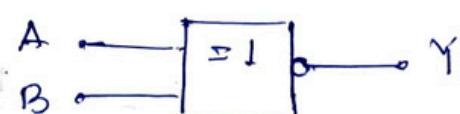

$$\bullet A = B \text{ o/p} = 1$$

$$A \neq B \text{ o/p} = 0$$

• XNOR follows commutative, associative law.

• Enable - 0, inverter  
Enable - 1, buffer.

A	B	Y
0	0	1
0	1	0

A	B	Y
1	0	0
1	1	1

## Properties.

- i)  $A \odot A = 1$
- $A \odot \bar{A} = 0$
- $A \odot 0_A = \bar{A}$
- $A \odot 1_A = A$ .

ii)  $A \odot A \odot A = A$ .

$A \odot A \odot \dots$  n times

$= A$ , n is odd

$= 1$ , n is even


- iii) XOR & XNOR are complementary when even inputs & same when odd no. of inputs.

Eg.  $A \odot B \odot C = A \oplus B \oplus C$ .


$$A \odot B \odot C \odot D = \overline{A \oplus B \oplus C \oplus D}$$
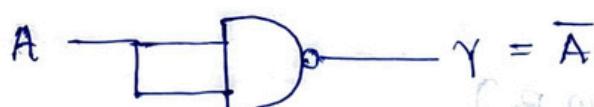
## \* NAND as Universal Gate.


- NAND as NOT.  $Y = \overline{AB}$ ,  $Y = \overline{AA} = \overline{A}$




- NAND as AND.

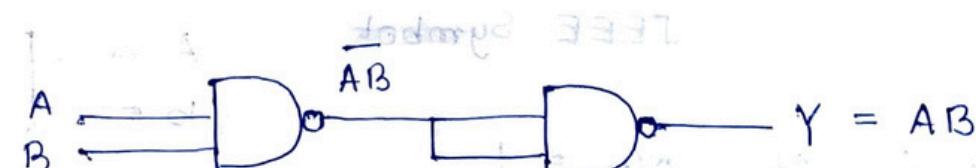

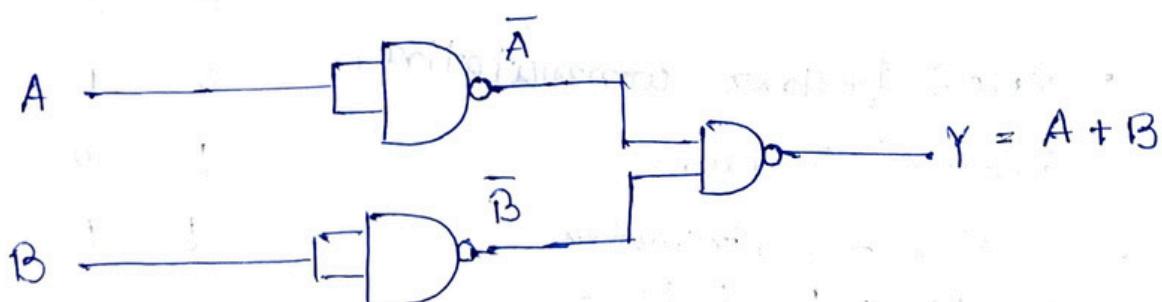- NAND as OR.  $Y = \overline{AB} = \overline{A} + \overline{B}$




• NAND as NOR.

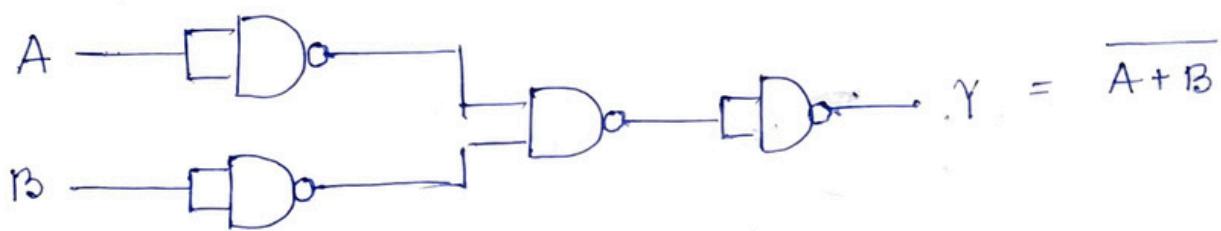


\* \* • NAND as XOR.

$$Y = A\bar{B} + \bar{A}B.$$

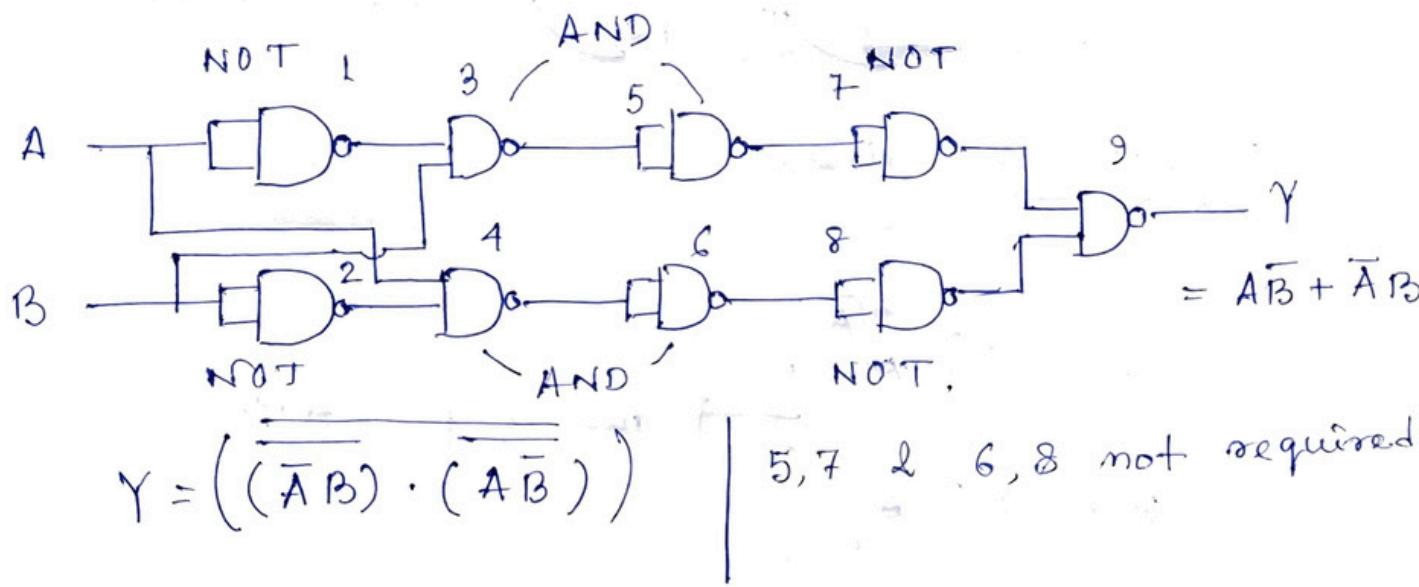


III

\* \* \*

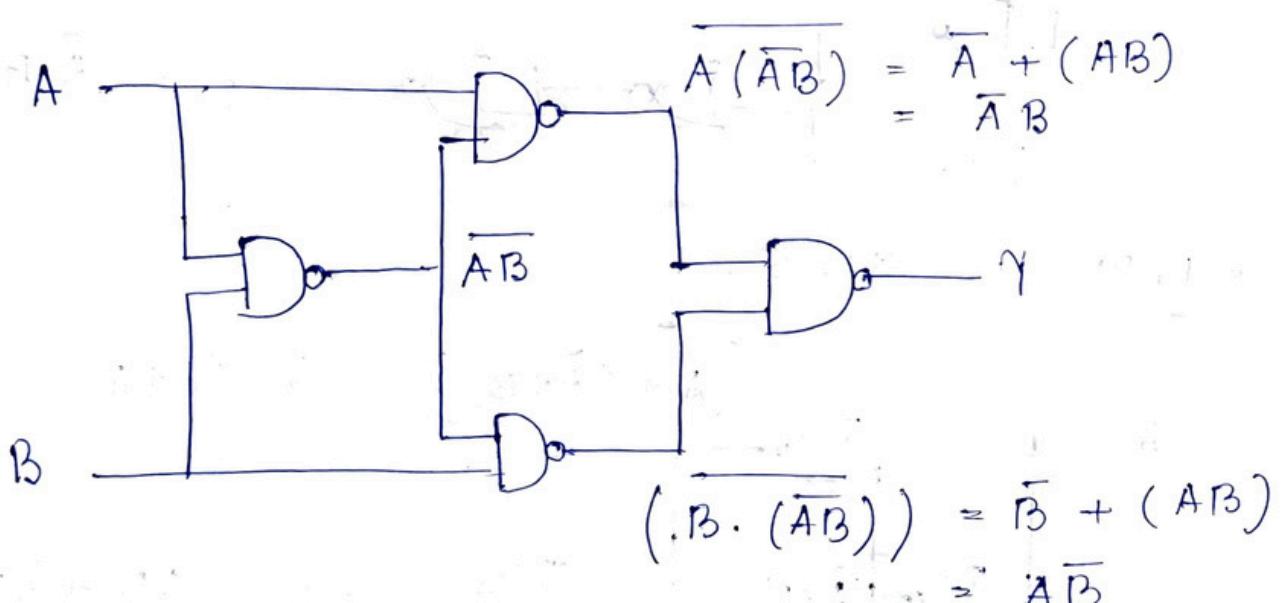


• NAND as XNOR.

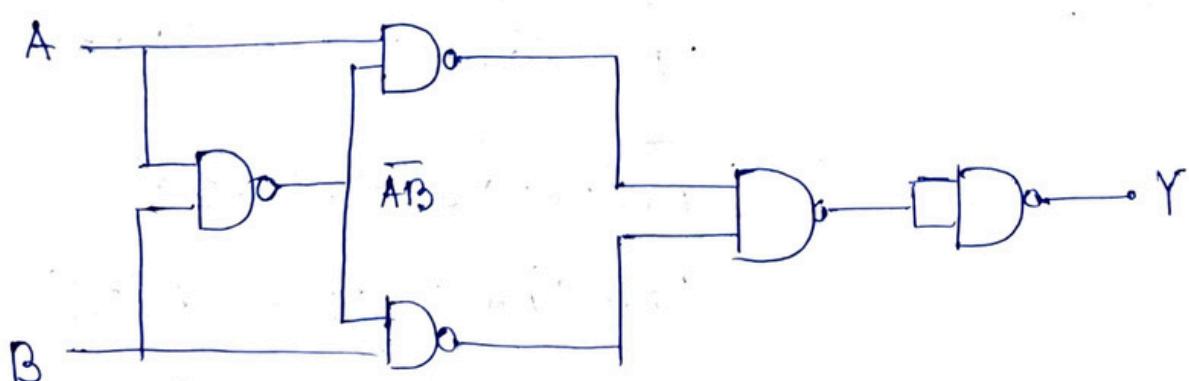

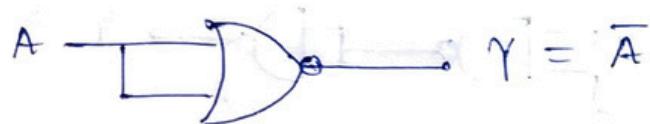
## \* NOR as Universal Gate.


- NOR as NOT.  $Y = \overline{A+B}$   $\gamma = \overline{A+A} = \overline{A}$




- NOR as OR.

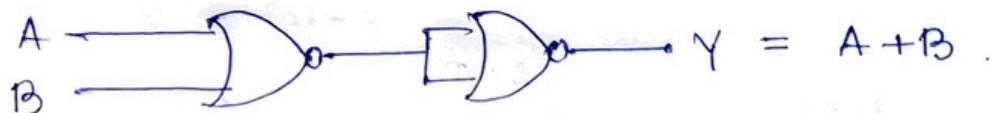


- NOR as AND.

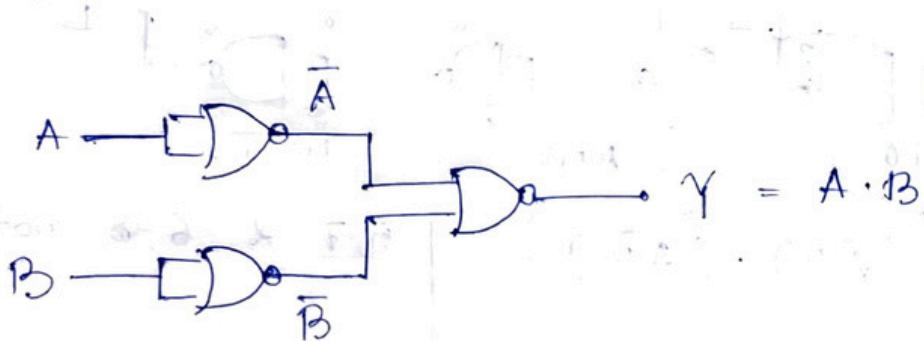

- NOR as NAND.

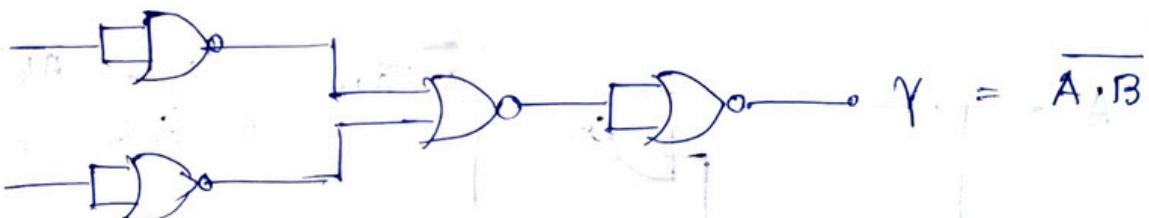

- NOR as XNOR.

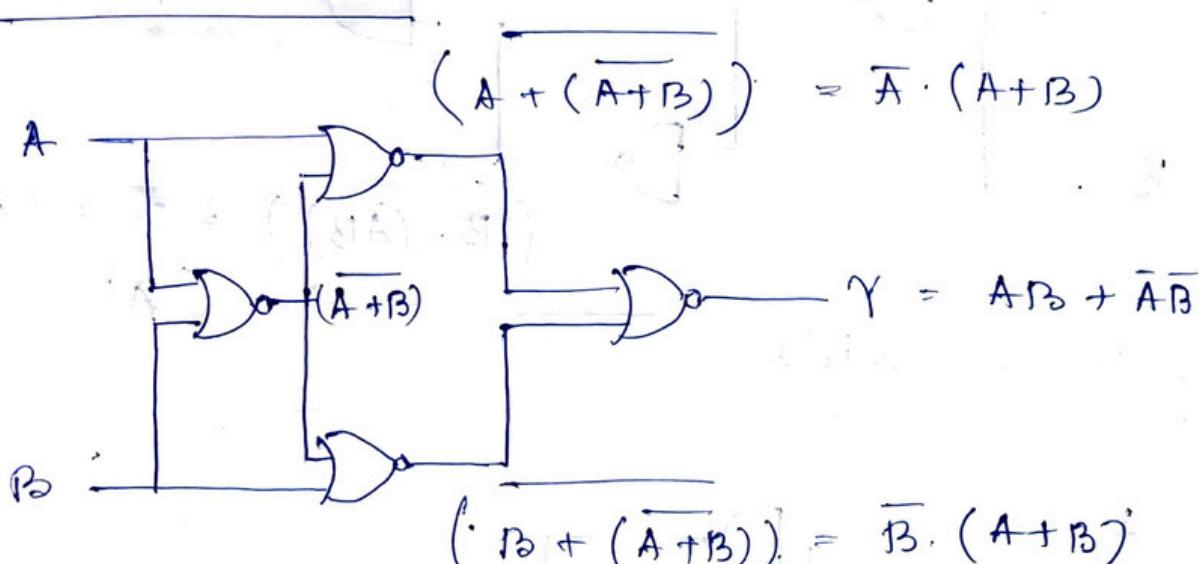


$$\therefore [A \cdot (A+B) + \bar{B} \cdot (A+B)]$$

$$= (A + (\overline{A+B})) \cdot (B + (\overline{A+B}))$$

$$\Rightarrow AB + (\overline{A+B}) = AB + \overline{AB}$$

• NOR as XOR.

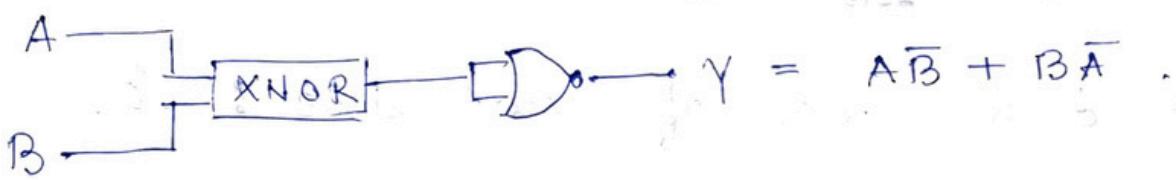

## \* Karnaugh Map [K' Map]

Eg.  $f = A + BC$ . In K' Map the adjacent cells are like only one variable should change.

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

A	BC	00	01	10	11
0	00	m <sub>0</sub>			
0	01		m <sub>1</sub>		
0	10			m <sub>2</sub>	
0	11				m <sub>3</sub>
1	00		m <sub>4</sub>		
1	01			m <sub>5</sub>	
1	10			m <sub>6</sub>	
1	11				m <sub>7</sub>

BC	00	01	11	10
A=0	m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>
A=1	m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>

Rule of adjacency.

Rolling of K' Map.

$$f = \overline{ABC} + A\overline{B}\overline{C} + A\overline{B}C + A\overline{B}C + ABC.$$

$$= \overline{ABC} + A\overline{B} + AB$$

$$= \overline{ABC} + A$$

$$= A + B\overline{C}$$

BC	00	01	11	10	group of 1's
A	0	0	0	1	m <sub>2</sub>
MSB	0	m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	

pairing : 2 1's, 4 1's, 8 1's,

16 1's

(No diagonal pairing, as adjacency not follows).

Same 1 can be paired more than once.

$$f = I + II$$

$$= A \cdot J \cdot J + J \cdot B \cdot \overline{C}$$

$$= A + B\overline{C}$$

If variable changes  $\rightarrow 1$

If not  $\rightarrow X/\bar{X}$ .

$$\text{Eg. } f(A, B, C) = \sum m(1, 3, 5, 7).$$

↓  
MSB      ↓  
LSB.      ↓  
SOP.

(i) Find out no. of variables : 3.

(ii) No. of cells in K'Map :  $2^3 = 8$ .

		BC	00	01	11	10
		A	0	1	1	0
0	1	0	m <sub>0</sub>	m <sub>1</sub>	m <sub>2</sub>	m <sub>3</sub>
		1	m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>

(iii) Pair 1's.

$$f = c \quad \text{Ans.}$$

$$\text{Eg. } f(A, B, C) = \sum m(0, 1, 2, 4, 7).$$

		BC	00	01	11	10
		A	0	1	0	1
0	1	1	1	0	1	1
		1	0	1	0	1

$$f = \bar{A}\bar{B} + \bar{B}\bar{C} + AB\bar{C} + \bar{A}\bar{C}. \quad (\text{Ans.})$$


$$\text{Eg. } f(A, B, C) = \sum m(1, 3, 6, 7).$$

		BC	00	01	11	10
		A	0	1	1	1
0	1	1	1	1	1	1
		1	1	1	1	1

$$f = \bar{A}C + BC + AB$$

$$\geq AB + \bar{A}C \quad [\text{by Redundancy Theorem}]$$
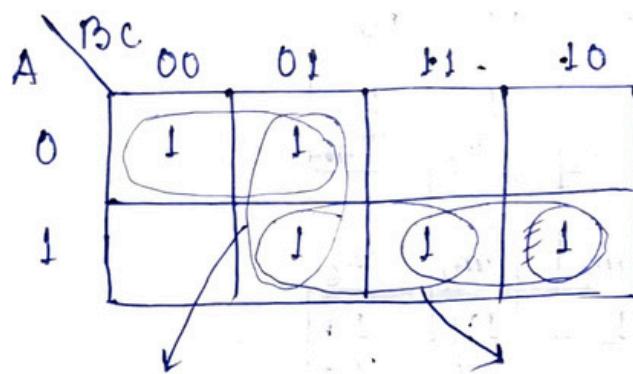
$$\text{Eg., } F(A, B, C) = \sum m(0, 1, 5, 6, 7).$$



$$F = \overline{A}\overline{B} + \overline{B}C + AB \quad | \quad F = \overline{A}\overline{B} + AC + AB$$


Result is minimum, but may not be unique.

• Implicants: Group of 1's in K' Map.


Prime Implicants: Largest possible group of 1's.

Essential Prime Implicants: At least one, there is a single one(s) which can not be combined in any other way.

Eg,

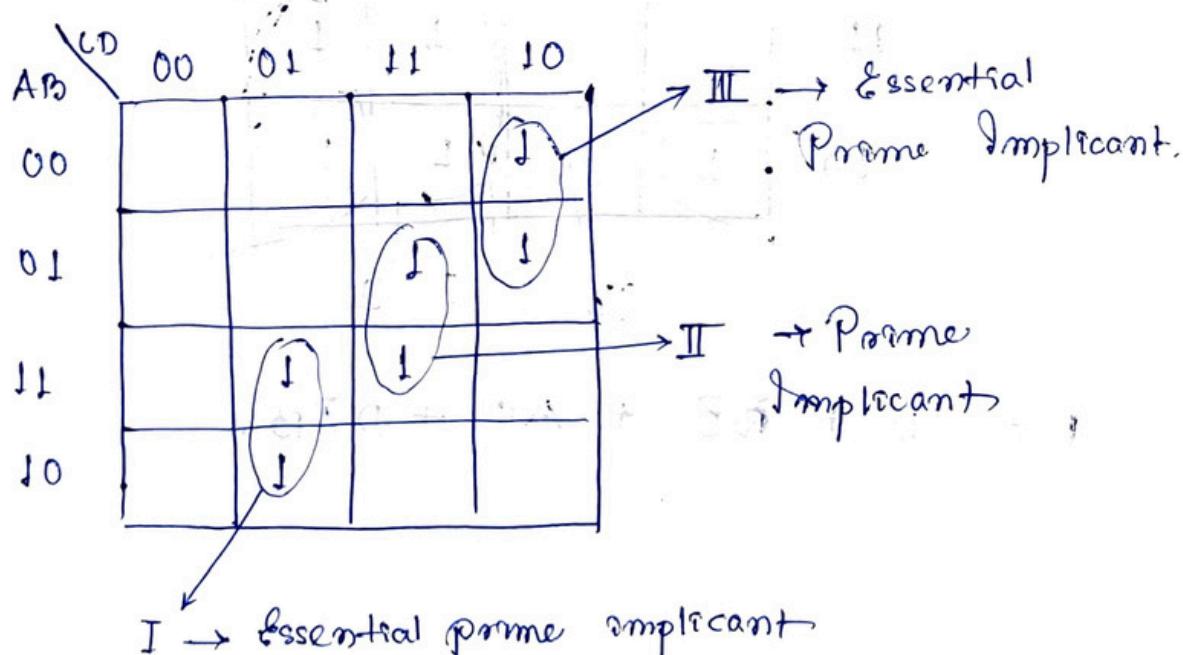
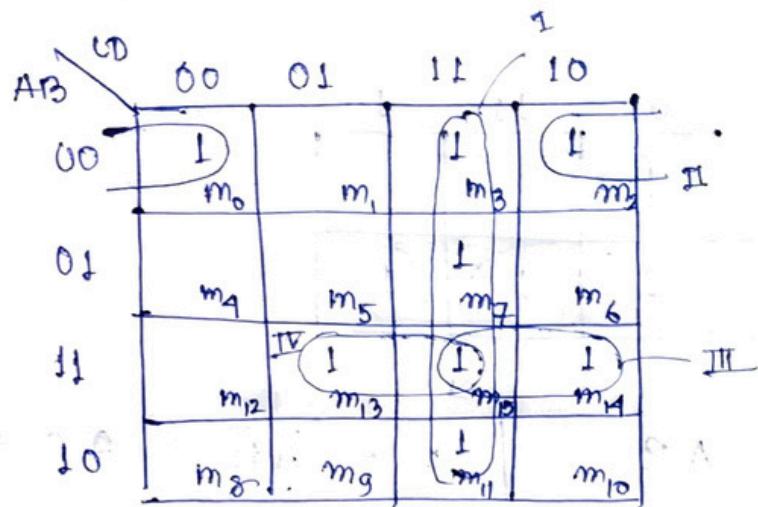
$$\text{Eq. } f(A, B, C, D) = \sum m (0, 2, 3, 7, 11, 13, 14, 15).$$



$$f = CD + \bar{A}\bar{B}\bar{D} + ABC + ABD.$$


- NB - Combining 2 1's  $\rightarrow$  1 interval is reduced

$$m \quad 4 \quad 1\text{'s} \rightarrow 2 \quad n \quad n \quad n$$

$$m \quad 8 \quad 1\text{'s} \rightarrow 3 \quad n \quad n \quad n$$

$$m \quad 16 \quad 1\text{'s} \rightarrow 4 \quad n \quad n \quad n$$


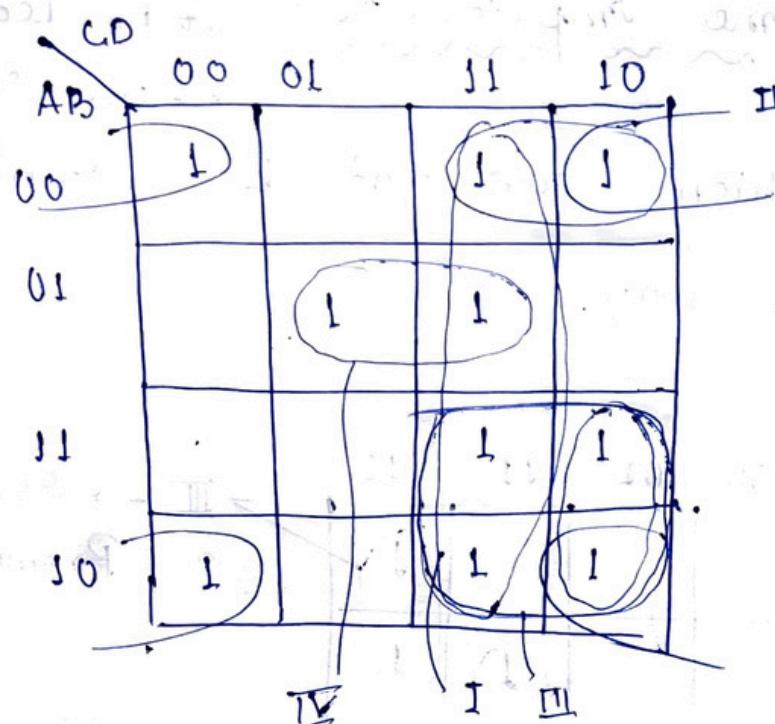
$$\text{Eq. } f(A, B, C, D) = \sum m (0, 2, 3, 5, 7, 8, 10, 11, 14, 15).$$



0010  
0000  
1000  
1010

$$f = CD + \bar{B}\bar{D} + AC + D\bar{A}B.$$
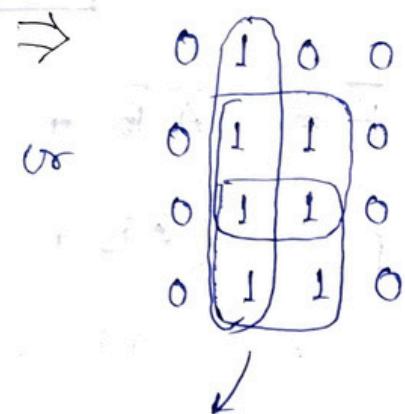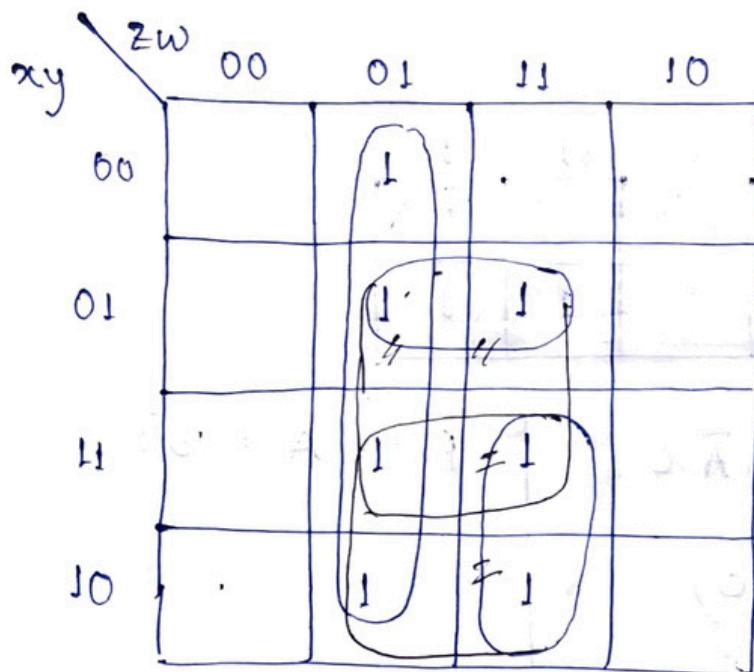
$$\text{Eg. } F(x, y, z, w) = \sum m (1, 5, 7, 9, 11, 13, 15).$$



$$F = xw + yw + \bar{z}w.$$


\* Don't Care in K' Map:

$$\text{Eg. } F(A, B, C) = \sum m (2, 3, 4, 5) + \sum d (6, 7).$$

, . . . , don't care

$d \rightarrow 0 \text{ or } 1.$

		BC	00	01	11	10	
		A	0	1	0	1	1
		A	1	1	1	$x_{m_7}$	$x_{m_6}$

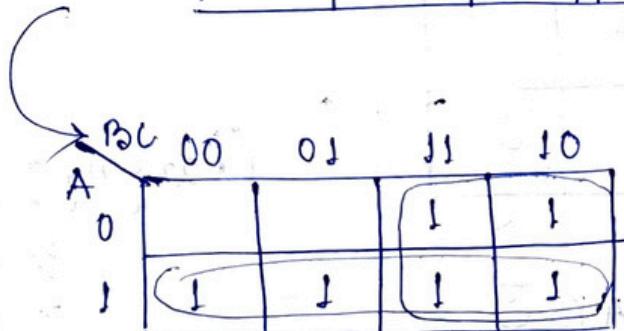

We take don't care as 1, when reducing using minterms, & take as 0 when reducing using maxterms.

$$F = A + B$$

\* K' Map using Maxterms.

Eg.

		BC	00	01	11	10
		A	0	0	0	1
			1	1	1	1
0	0	0	0	0	0	1
1	0	1	1	1	1	1

$$\bar{F} = \overline{AB} + \overline{AC}$$

$$F = A + BC$$

$$F = (\overline{AB} + \overline{AC})'$$

$$= \overline{AB} \cdot \overline{AC}$$

$$= (A+B) \cdot (A+\overline{C})$$

$$= A + BC$$

Complementing

Eg.  $f(A, B, C, D) = \sum_m (1, 3, 4, 5, 9, 11, 14, 15)$

$$= \prod M (0, 2, 6, 7, 8, 10, 12, 13)$$

		CD	00	01	11	10
		AB	00	0	0	0
			01			0
0	0	00	0	0	0	0
0	1	01			0	0
1	0	11	0	0	0	0
1	1	10	0		0	0

complement  $\bar{F} = \overline{BD} + \overline{ABC} + A\overline{BC}\overline{C}$


Changing + → ·  
· → +

$$\overline{x} \rightarrow x$$

$$x \rightarrow \overline{x}$$

$$F = (B+D) \cdot (A+\overline{B}+\overline{C}) \cdot (\overline{A}+\overline{B}+C)$$

\* K' Map with 5 variables:

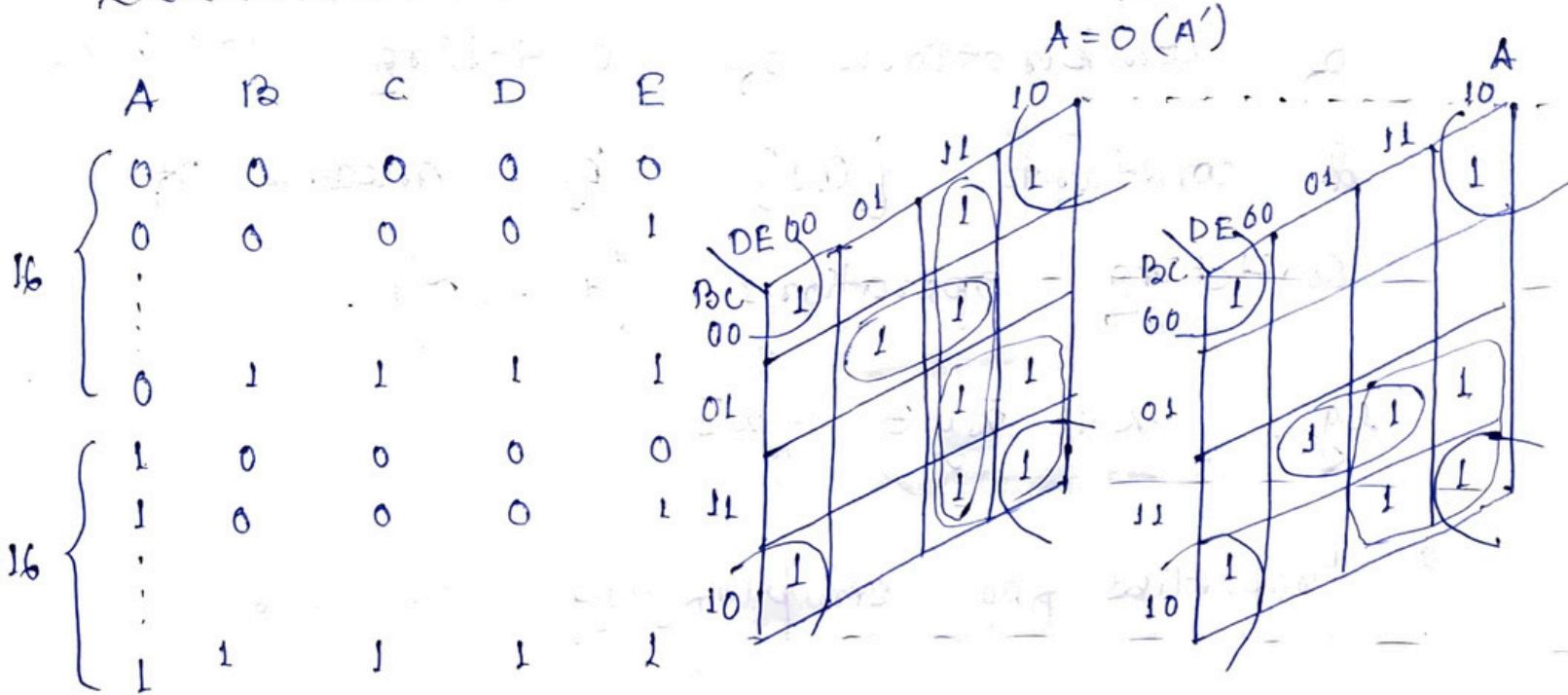

$$F = \bar{C}\bar{E} + BD + \bar{A}DE + \bar{A}\bar{B}CE + ABGE$$

## Switching Algebra.

\* Idempotency :

$$x \cdot x = x$$

$$x + x = x$$

$$x + 1 = 1 \quad x \cdot 0 = 0$$

$$x + 0 = x \quad x \cdot 1 = x$$

\* Commutativity :

$$x + y = y + x$$

$$xy = yx$$

\* Associativity :  $((x+y)+z) = (x+(y+z))$

$$(x \cdot y) \cdot z = x \cdot (y \cdot z)$$

\* Complementation :

$$x + \bar{x} = 1$$

$$x \cdot \bar{x} = 0$$

\* Distributivity :  $x \cdot (y+z) = x \cdot y + x \cdot z$

$$x + y \cdot z = (x+y) \cdot (x+z)$$

\* Duality Principle

$$\begin{array}{cccc} \downarrow & \downarrow & \downarrow & \downarrow \\ + & \cdot & 1 & 0 \end{array}$$

\* Switching expression is a finite number of combinations of switching variables & constants  $\{0, 1\}$  by means of switching operations  $(+, \cdot, \sim)$ .

e.g.  $x + \bar{x}yz + x\bar{z}$

\* Properties for simplifying the SE:

1. Absorption:  $x + x \cdot y = x$

$$x + x' \cdot y = x + y$$

2. Dual:  $x \cdot (x' + y) = xy$

3. Consensus theorem:

$$xy + \bar{x}z + yz = xy + \bar{x}z$$

Proof

$$\begin{aligned} & xy + \bar{x}z + yz \\ &= xy + \bar{x}z + xyz + \bar{x}yz \\ &= xy(1+z) + \bar{x}z(1+y) \\ &= xy + \bar{x}z. \end{aligned}$$

e.g.  $x'y'z + yz + xz$ .

$$= z(x'y' + y + x)$$

$$= z[(x'y') (y + y') + x]$$


$$= z(x'y' + y + x)$$

$$= z.$$

\* De Morgan's Law:

$$\overline{xy} = \bar{x} + \bar{y}$$

$$\overline{x+y} = \bar{x}\bar{y}$$

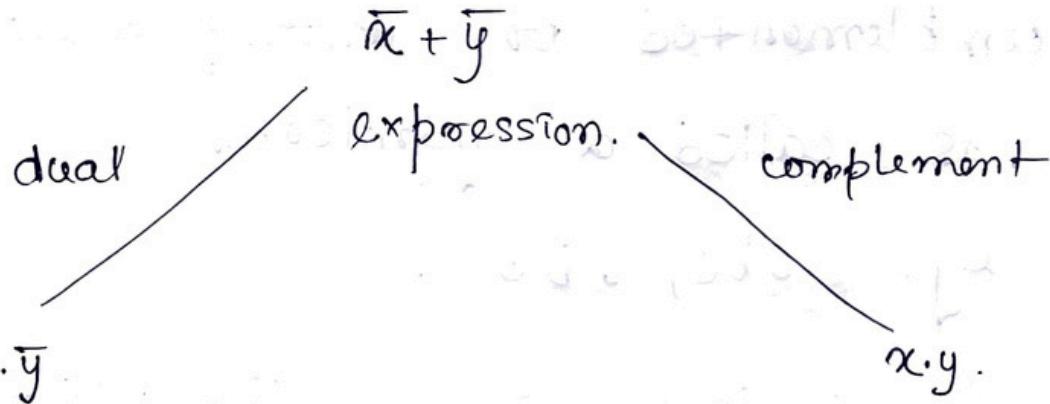

~~Imp~~ \* eg.

$$\begin{aligned}
 & (x+y) [x'(y'+z')]' + x'y + x'z' \\
 &= (x+y) [x + (y'+z')'] + x'y + x'z' \\
 &= (x+y) [x + \underline{yz}] + x'(y'+z') \\
 &= x + (yz) + x'y' + x'z' \\
 &= (x+x')(x+y') + yz + x'z' \\
 &= x+y' + yz + x'z' \\
 &= x + z' + y' + yz \\
 &= x + z' + y' + z \\
 &= 1.
 \end{aligned}$$

## \* Canonical forms:

→ A product term which contains each of  $n$  variables as factors either in complemented or uncomplemented form, is called a min-term.

e.g.  $abc, ab'c$ .

→ A min-term given the value 1 for exactly one combination of the variables.

→ The sum of all min-terms of  $f$  for which  $f$  assumes 1 is called canonical sum of products or disjunctive normal form.

$$a + bc + ac \quad \text{SOP}$$

$$abc + \bar{a}bc \quad \text{Canonical SOP.}$$

→ To find canonical SOP, take the sum of product terms of literals when the function value is 1.

→ A sum term that contains each of  $n$  variables as factors either in complemented or uncomplemented form is called maxterm.

$$\text{eg. } (A + \overline{B} + C)(A + B)$$

→ A maxterm gives the value 0 for exactly one combination of the variable.

→ The product of all maxterms of  $f$  for which  $f$  assumes 0 is called canonical product of sums or conjunctive normal form.

$$(A + B)(B + C) \quad \text{POS.}$$

$$(A + B + C)(A + \overline{B} + \overline{C}) \quad \text{Canonical POS.}$$

→ To find canonical POS form of  $f$ , take the maxterms of literals when value of  $f$  is 0.

\* SOP minterm  $f$  is high (1)  $\Sigma$

POS maxterm  $f$  is low (0)  $\Pi$